

This article collates design information on the 1949 'new' Williamson amplifier circuit. By detailing design considerations of the original circuit, assessment of altered operating conditions or part selection or circuit changes can be made.

A listing and commentary of changes proposed over decades by magazine articles and manufactured clones is provided.

The aim of this article is not to propose substantial changes to the original circuit, but rather to appreciate the original circuit's design outcomes, and why some have made changes to the design over time.

Contents

- 1. Preamble 1
- 2. Mid-band behaviour 2
- 3. Low-frequency behaviour..... 3
- 4. High-frequency behaviour..... 5
- 5. Power Supply..... 9
- 6. Signal stage valve types and bias conditions..... 12
- 7. Output stage bias conditions..... 15
- 8. Changes 19
- 9. Setup and Testing..... 26
- 10. References 27

1. Preamble

The 1949 Williamson 'new' amplifier circuit with 6SN7 and KT66 valves, and Partridge WWFB output transformer, is the default circuit assessed here (807 related parameters given in {brackets}). The circuit schematic shows idle condition voltages and currents (the first stage power supply voltage is ~305V, not 320V, and the driver stage power supply rail is ~430V). A Partridge WWFB/1/0.95 is configured as 8.5Ω (3 secondary sections in series). At 15W output, the output voltage is 11.3Vrms.

Williamson related articles and information are collated at <http://dalmura.com.au/projects/Williamson.php>. Valve related parameters identified in this article may differ between datasheets, and hence various values may not exactly align with all datasheets or reference articles.

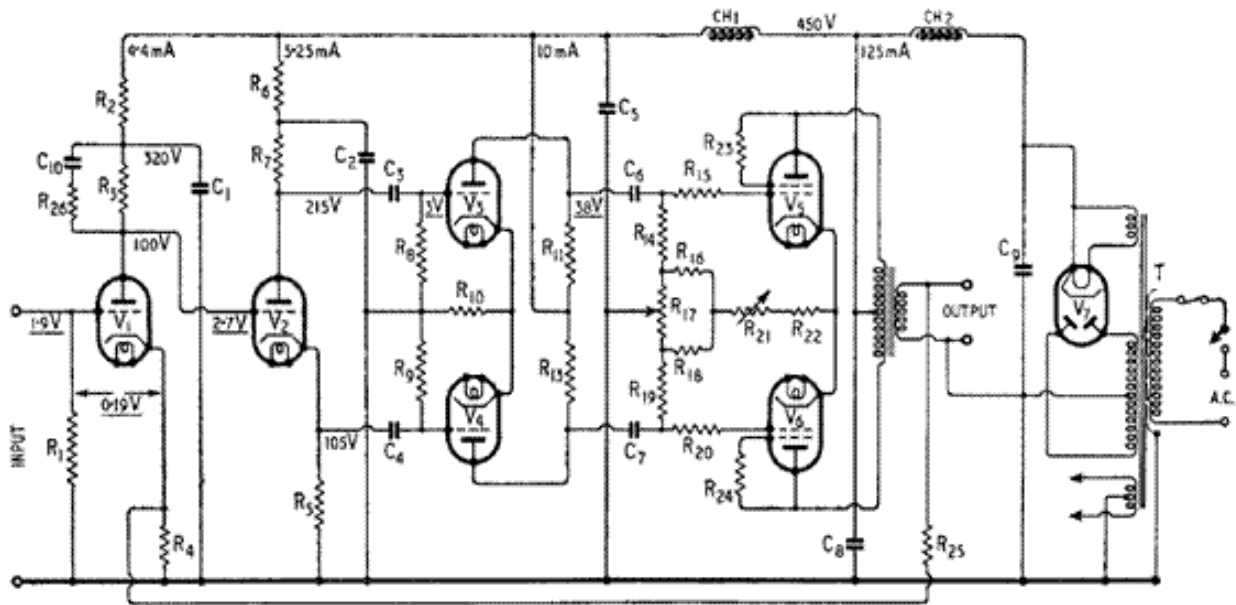


Fig. 1. Circuit diagram of complete amplifier. Voltages underlined are peak signal voltages at 15 watts output.

| | | |
|---|---|---|
| R_1 1MΩ ½ watt ± 20% | R_{14}, R_{19} 0.1MΩ ½ watt ± 10% | C_9, C_7 0.25µF 350V wkg. |
| R_2 33,000Ω 1 watt ± 20% | R_{15}, R_{20} 1,000Ω ½ watt ± 20% | C_9 8µF 600V wkg. |
| R_3 47,000Ω 1 watt ± 20% | R_{16}, R_{18} 100Ω 1 watt ± 20% | C_{10} 200pF 350V wkg. |
| R_4 470Ω ½ watt ± 10% | R_{17}, R_{21} 100Ω 2 watt wirewound variable | CH_1 30H at 20mA |
| R_5, R_7 22,000Ω 1 watt ± 5% (or matched) | R_{22} 150Ω 3 watt ± 20% | CH_2 10H at 150mA |
| R_6 22,000Ω 1 watt ± 20% | R_{23}, R_{24} 100Ω ½ watt ± 20% | T Power transformer |
| R_8, R_9 0.47MΩ ½ watt ± 20% | R_{26} 1,200 √ speech coil impedance ½ watt (see table) | Secondary 425-0-425V 150 mA, 5V. 3A, 6.3V 4A, centre-tapped |
| R_{10} 390Ω ½ watt ± 10% | R_{25} 4,700Ω ½ watt ± 20% | V_1, V_2 2× L63 or 6J5, 6SN7 or 6B5 |
| R_{11}, R_{13} 47,000Ω 2 watt ± 5% (or matched) | C_1, C_2, C_6, C_8 8µF 500V wkg. | V_3, V_4 do. do. |
| | C_3, C_4 0.05µF 350V wkg. | V_5, V_6 KT66 V_7 Cossor 53KU, 5V4 |

Figure 1. 1949 'new' Williamson amplifier schematic circuit

2. Mid-band behaviour

A feedback voltage V_{fb} is applied by R4-R25 divider from the amplifier output, with a feedback parameter $\beta = R4/(R4+R25)$. R4 also carries the V1 anode signal current, which provides some current feedback, and although this is significant ($R4 \sim 1/gm$ of V1), it is often ignored for expediency. R4 and R25 also set the V1 bias – see later section.

$$V_{gk} = V_{in} - V_{fb} = V_{in} - \beta \cdot V_{out}$$

signal input is feedback voltage added to V1 grid-cathode voltage

$$V_{out} = A_o \cdot V_{gk}$$

A_o is the open loop gain from input stage V_{gk} to V_{out} (R4 bypassed to ground) for AC signals.

$$A_v = V_{out} / V_{in} = A_o / (1 + \beta \cdot A_o)$$

A_v is the closed loop total amplifier gain with feedback applied.

The first stage includes the global negative feedback connection, with the stage gain dependant on whether the feedback loop is closed or not.

- 6SN7 @ $I_p=4.4mA$, $E_b=100V$: $R_i \sim 9.2k$, $g_m \sim 2.2ms$, $\mu=20$
- The shelf network C10-R26 is considered an open circuit.
 - Only R3 loads the stage
- Stage gain $A_1 = V_{o1} / V_{gk}$

$$= \mu \cdot R_3 / (R_i + R_3) = 16.7 \text{ (24.5dB)}$$
 - Gain with R4 signal bypassed to ground
- Stage gain $A_1' = V_{o1} / V_{in} = A_1 / 10 = 1.67 \text{ (4.5 dB)} = \mu \cdot R_3 / (R_i' + R_3)$
 - Gain with 20dB feedback connected
 - Hence $R_i' = R_3 \cdot (10 \cdot \mu / A_1 - 1) = 11 \times 47k = 517k$
- Stage gain $A_1'' = V_{o1} / V_{in}$ (R25 disconnected, and not grounded)

$$= \mu \cdot R_3 / (R_3 + R_i + (\mu+1) \cdot R_4) = 20 \times 47k / (47k + 9k + 21 \times 470)$$

$$= 940k / 66k = 14.3 \text{ (23dB)}$$
 - V_{in} includes voltage across R4, but no feedback from output
 - eg. low or high frequency operation
 - $R_i'' \sim R_i + (\mu+1) \cdot R_4 = 9.2k + 9.9k = 19.1k$
 - Quasi-open-loop circuit configuration

The phase splitter stage

- 6SN7 @ $I_p=5.2mA$, $E_b=110V$: $R_i \sim 9k$, $g_m \sim 2.3ms$, $\mu=20$
- Total stage output loading $R = R_7 // R_8 = 21k\Omega$
- Stage gain $A_2 = \mu \cdot R / (R_i + R(\mu+2)) \sim 0.89 \text{ (-1 dB)}$

The driver stage

- 6SN7 @ $I_p=5mA$, $E_b=215V$: $R_i \sim 9k$, $g_m \sim 2.3ms$
- Stage gain $A_3 = g_m \cdot (R_i // R_{11} // R_{14}) = 2ms \times 9k / 47k // 100k = 2 \times 7.0 = 14 \text{ (23 dB)}$
- Fig.1 schematic shows driver stage gain $A_3 = 38/3 = 12.7$

Output stage including output transformer

- 26.9Vrms on KT66 grid (38Vpk at 15W output with 40VDC cathode bias from [1])
- 11.3Vrms on speaker load (15W output at 8.5Ω load)
- Transformer turns ratio $V_{out}/V_{plate} = A_5 = 2 \times \sqrt{(8.5/10k)} = (\sqrt{Z_o})/50 = 1/17 \text{ (-24.6dB)}$
- $V_{plate} = 11.3V \times 17 = 192V_{rms}$
 - See Figure 12 for loadline showing $\sim 192V \times \sqrt{2} = 270V_{pk}$ swing from bias point to $V_g \sim 0V$.
- Stage gain $A_4 = 192V/26.9V = 7.14 \text{ (17 dB)}$

The open-loop amplifier gain $A_o = A_1 \cdot A_2 \cdot A_3 \cdot A_4 \cdot A_5 = 16.7 \cdot 0.89 \cdot 14 \cdot 7.14 / 17 = 87.4 \text{ (38.8 dB)}$.

- Based on R4 in circuit but bypassed, and with R25 disconnected.
- [2] identifies drooping open-loop gain above about 8W output with no feedback.
 - Likely due to 807 grid conduction ($V_{gk} < 0$ but non-zero current), or driver stage approaching swing limits.

From [1], the measurement of loop gain is made by disconnecting the feedback resistor R25 from first stage cathode, and connecting it to ground via a 470Ω resistance, and measuring the signal voltage across that 470Ω. The open-loop amplifier plus feedback gain is then set to 10 (20 dB) = $A_o.R4/(R4+R25)$. It is assumed that the input stage has R4 bypassed for this setup procedure, but that is not explicitly stated in [1].

Figure 1 assessment [23] of AC peak signal levels identifies the following:

- V1 plate current AC signal: $2.7V_{pk}/47k\Omega = 0.057mA_{pk}$
- V1 AC resistance loading the cathode: $R_k = (R3+Ri)/(\mu + 1) = (47k+9.2k)/21 = 2.68k\Omega$
- Feedback voltage across R4 and Rk: $1.9V - 0.19V = 1.71V_{pk}$.
- Signal current through Rk: $1.71V/2.68k\Omega = 0.638 mA_{pk}$ in Rk.
- Signal current in to R4-R25 node: $0.638mA - 0.057mA = 0.581 mA_{pk}$.
- R4-R25 node currents: $0.581 mA_{pk} = (\sqrt{2} \times 11.3V - 1.71V)/R25 - 1.71V/R4$
- Hence $R25 = (16V - 1.7V) / (0.581mA + 3.64mA) = 14.3V / 4.22mA = 3.4k\Omega$
- The calculated value of R25 is the same as the parts list value of $1200 \times \sqrt{(8.5\Omega)} = 3.5k$.

Alternative approximation:

- The input signal sensitivity for 15W output is $11.3V/7.1 = 1.6V_{rms}$.
- The schematic indicates the closed-loop amplifier gain A_v is $11.3V_{rms}/(1.9V_{pk}/\sqrt{2}) = 8.4$ (18.5dB).
- Feedback parameter $\beta = R4/(R4+R25) = 10/A_o = 0.114$ (-18.8 dB) from [1]
 - $A_o = 87.4$ (38.8 dB).
- The closed-loop amplifier gain $A_v = A_o/(1+\beta.A_o) = 87.4/(1+0.114 \times 87.4) = 7.95$ (18dB).
 - So the circuit has about $A_o - A_v = 38.8dB - 18dB = 20.8 dB$ of global midband feedback.
- $R25 = (87.4 \times 470/10) - 470 = 3.64k\Omega$.
 - The calculated value of R25 is the same as the parts list value of $1200 \times \sqrt{(8.5\Omega)} = 3.5k$.
 - Parts list value appears to be an approximation:
 - $R25 = A_o.R4/10 - R4$

$$\sim 47.A1''.A2.A3.A4.(\sqrt{Z_o}) / 50$$

$$= 1195.\sqrt{Z_o}$$

3. Low-frequency behaviour

Low frequency behaviour of the Williamson amp is dominated by CR high-pass filter coupling between stages, and the output stage RL high-pass filter due to output transformer inductance, with the addition of other CR power supply decoupling effects. The close proximity of the two highest pole frequencies indicates possible instability as phase margin at 20dB FB is likely to be quite small, and requires the zeros to assist the phase margin, with transformer pole likely to be moving around with signal level. Poor output stage static balance could easily raise the transformer pole frequency to equal or exceed the two dominant poles.

Corner frequency summary:

- | | | |
|---------------------------------------|-----------------------|-----------------|
| a) Phase splitter stage CR coupling | 6.8 Hz pole | |
| b) Driver stage CR coupling | 6.4 Hz pole | |
| c) Output stage with transformer | 3.9 Hz pole (nominal) | {4.7Hz} |
| d) Phase splitter stage B+ decoupling | 0.9 Hz zero | |
| e) First stage B+ decoupling | 0.6 Hz zero | +18dB gain lift |

Williamson reported a low frequency phase shift of 90deg and -3dB at ~10 Hz for open-loop operation. For 20dB of feedback, Figure 2 indicates a phase margin of 20-30 deg at 10Hz, and gain margin of 8dB at 2Hz.

- a) Phase splitter stage output CR coupling: $50\text{nF}-470\text{k}\Omega = 6.8\text{Hz}$ HPF
- b) Driver stage output CR coupling: $250\text{nF}-100\text{k}\Omega = 6.4\text{Hz}$ HPF
- c) Output transformer response:
 - transformer PP inductance varies with:
 - idle DC current imbalance.
 - signal level excitation.
 - signal level valve conductance imbalance (causing a DC offset).
 - transformer core characteristics, including clamping and T-U lamination edge butting.
 - KT66 triode plate resistance $\sim 1.45\text{k}\Omega$ [Va=400V, Vg1=-38V, Ia~71mA]
 - Constant cathode voltage assumed.
 - {~ 1.9k Ω }
 - corner frequency is at most $(10\text{k}\Omega / (2 \times (1.45\text{k} + 202))) / (2\pi \times 100\text{H}) = 3.9\text{Hz}$ HPF {4.7Hz}
 - 5VAC excitation rated [1] minimum 100H PP inductance used, for small signal condition.
 - At higher signal level, L will be higher and corner frequency will reduce.
 - At lower signal level, or when some DC imbalance exists, L will be lower and corner frequency will increase.
 - Primary winding DCR included.
 - 10k Ω PP reflected loading from speaker side assumed.
 - 10k Ω secondary loading is about 3x the primary side source resistance ($2 \times (1.45\text{k} + 202) = 3.3\text{k}\Omega$), which defines the nominal roll off rate about the corner frequency. The roll-off rate is significantly faster if secondary loading increases. [18]
- d) Phase splitter stage supply R6-C2 decoupling: $22\text{k}\Omega-8\mu\text{F} = 0.9\text{Hz}$ LPF
 - At DC, the phase splitter anode loading increases from 22k to 44k, introducing phase splitter output gain imbalance.
- e) First stage supply R2-C1 decoupling: $33\text{k}\Omega-8\mu\text{F} = 0.6\text{Hz}$ LPF
 - Stage gain at mid-band $A1 = \mu \cdot R3 / (Ri' + R3) = 1.67$ (4.5 dB)
 - Stage gain at low frequency $A1'' = \mu \cdot R3 / (Ri'' + R3) = 14.3$ (23 dB)
 - Stage gain at DC $A1\text{dc} = \mu \cdot (R3 + R2) / (Ri'' + R3 + R2) = 20 \times 88\text{k} / (19\text{k} + 88\text{k}) = 16.4$ (24.3 dB)
 - At DC, the first stage gain is increased by ~20dB

Note that as the frequency reduces below 1Hz, the first stage and phase splitter stage lose the benefit of local supply decoupling due to the rising impedance of C1 and C2. The impedance of C5 is similarly rising, and so the stages share additional loading from CH1. The signal currents through V1 and V2 are in antiphase and of similar magnitude, so effectively cancel each other at the C5 node.

The preferred method to alleviate LF instability using a shelf network is described in 8 c).

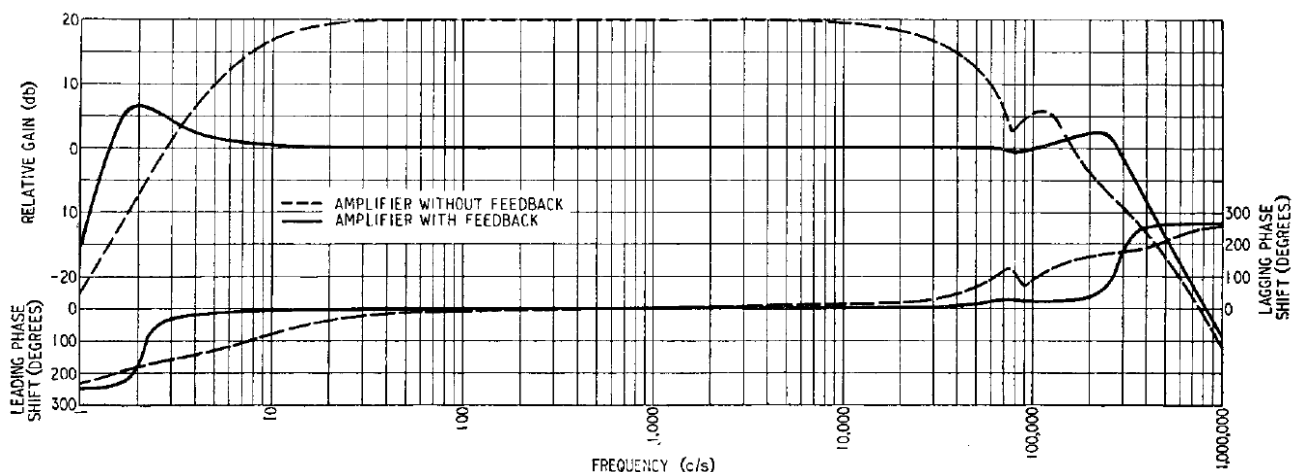


Figure 2. Loop gain and phase-shift characteristics of amplifier

4. High-frequency behaviour

High frequency behaviour of the Williamson amp is dominated by the output transformer response, with the addition of multiple RC low-pass filter couplings due to inter-stage connections. Additional stray capacitance could significantly lower an RC corner frequency, such that phase margin is reduced. Parts and layout for the first stage to phase inverter stage, and the driver stage to output stage, are most susceptible.

Corner frequency summary:

| | | |
|-----------------------------------|-------------|-------------------|
| a) Transformer RLC | ~60 kHz | (2 pole roll-off) |
| b) First stage output RC | 450 kHz max | |
| c) Driver stage output RC | 550 kHz max | |
| d) Phase splitter stage output RC | 5.7 MHz max | |

Williamson reported a high frequency -3dB at ~30 kHz for open-loop operation, and phase shift of 90deg at ~50kHz, with a resonance amplitude dip at about 60kHz. The gain and phase curves in Figure 2 are for the 'improved' amplifier including the shelf network on the input stage, with a phase margin of 20-30deg at 150kHz, and a gain margin of 8dB at 300kHz.

- a) The output transformer causes the dominant low-pass filter response that dictates the high-frequency bandwidth limit and stability margins of the amplifier. The output stage valves represent a voltage source with series resistance that drives signal current through the OT primary winding, which can be simplistically represented by series leakage inductance and winding DC resistance, and then a parallel connection of the primary half-winding presenting the reflected load impedance, and a shunt lumped capacitance across the winding. The source resistance, and the shunt capacitance, leakage inductance and dc winding resistance introduce an RLC two pole roll-off with a damped response. In reality, the interleaving and sectioning required to minimise leakage inductance for both class A and AB operation, and even UL operation, make it difficult to present anything but a simplistic representation.

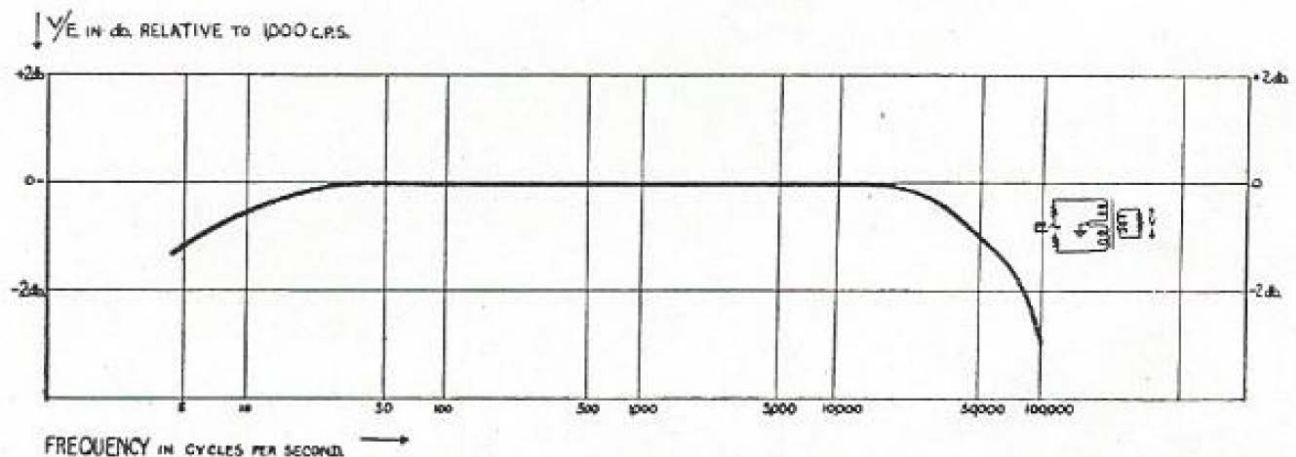


Figure 3. Partridge WWFB frequency response

The Partridge WWFB response [27] is with a $3k3\Omega$ source resistance (equivalent to the internal resistance of two series KT66 triodes) ($3k8\Omega$) and a $10k\Omega$ primary loading, and with 10W output. Lee [18] assesses the high frequency response for a step down audio transformer and provides response curves for when source resistance R_1 is half the primary loading R_2 , which can be compared to the WWFB response.

The WWFB datasheet provides a self capacity value of 500-580pF 'measured between either anode connection and the centre point of the primary commoned to the core and one point on the secondary'.

- The plate-to-CT (P-CT) lumped shunt capacitance C_p is measured using RC LPF -3dB frequency (F_{-3dB}) test setup, where R is $\sim 5x$ PP impedance and inserted in series with signal generator driving P-CT half-winding, with other P-CT open, and secondaries open and connected to CT and ground.
 - Measure the P-CT winding voltage, which should rise to a maximum in the kHz range, and then reduce to 71% of maximum at F_{-3dB} .

- Measured capacitance $C_p = 1/(2\pi \cdot F_{-3dB} \cdot R)$
- Subtract measurement voltmeter or oscilloscope probe capacitance off the measured capacitance.
- The lumped capacitance seen by the driving plate can become 2x P-CT capacitance if other PP valve enters cut-off (class B operation).

The capacitance C_p is assumed to represent the X_c reactance in Lee's model.

- $B = X_c/R_1 \sim 1/(2\pi \cdot 60kHz \cdot 500pF \cdot 3k3\Omega) = 1.6$, assuming $F_r = 60kHz$
- From Figure 4, high frequency response for step-down transformer for $R_2 = 2 \cdot R_1$ [17], $F_{-3dB} \sim 1.6 f/F_r$. So $F_{-3dB} \sim 1.6 \times 60kHz = 96kHz$. Which compares with datasheet frequency response.

The WWFB datasheet provides a leakage inductance "measured as a series element in the primary" of 15-20mH.

- Gilson's W01796A output transformer datasheet [31] indicates that the primary winding leakage inductance should aim to be less than 25% of the P-P load of 10kΩ at the edge of audio bandwidth (eg. 25kHz), which would require leakage inductance to be < 16mH.
- The CFB datasheet indicates that the WWFB has a half-primary leakage inductance of 900mH, where complementary half-primary is shorted. This leakage inductance is only of concern for class B operation.
- The CFB datasheet indicates the same frequency response is achieved, but with a slightly higher self capacitance (600pF), and a lower series leakage inductance (10mH).

The lumped shunt capacitance and leakage inductance should have a calculated resonance frequency $F_r = 1/[2\pi\sqrt{(L_p \cdot C_p)}]$ similar to a measured OT resonance frequency. Williamson identified a resonant frequency of about 60kHz. The WWFB calculated frequency is ~ 60kHz (500pF, 15mH), and the CFB calculated frequency is ~ 65kHz (600pF, 10mH).

The two-pole LC roll off reduces the open-loop gain by about 40dB over the decade from 60kHz to 600kHz, as indicated in Figure 2.

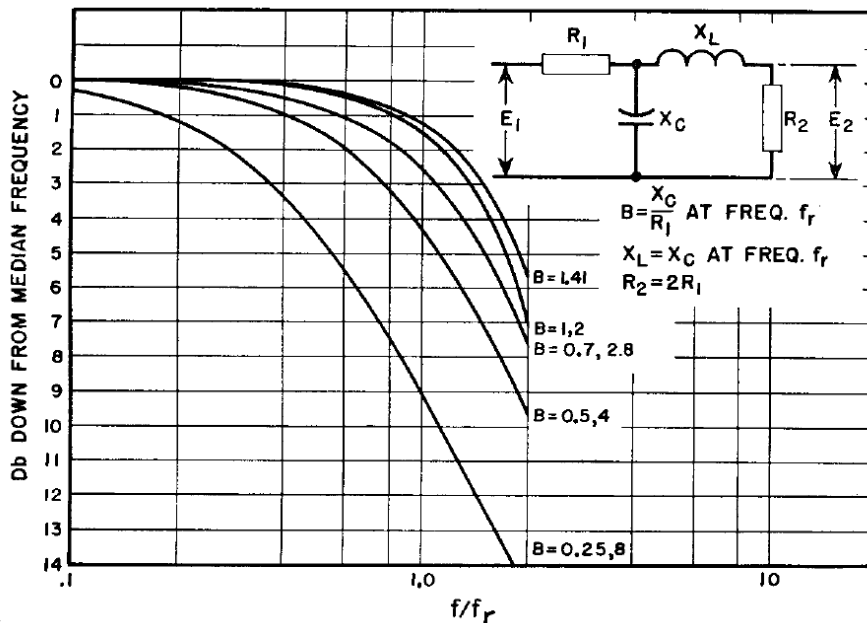


Figure 4 High frequency response for step-down transformer for $R_2 = 2 \cdot R_1$ [18]

- b) First stage RC roll-off due to effective output resistance and anode loading capacitance.
- First stage triode internal resistance R_i is increased by feedback signal at cathode. The effective first stage internal resistance is R_i' .
 - $R_i' = 517k$ see mid-band section
 - $R = R_a.R_i'/(R_a+R_i')$ [$R_a=47k$]
 $= 43k$
 - First stage output loading capacitance.
 - First stage triode anode capacitance to cathode and heater
 - 0.7pF for 6SN7
 - Some valve holder parasitic capacitance as plate pin is adjacent to cathode
 - Parasitic capacitance should be low for dual triode 6SN7, due to direct anode to grid link.
 - Capacitance from shelf network across plate 47k not included here.
 - Phase splitter stage triode grid capacitance.
 - $C_{gk} = 2.6pF$
 - $C_{gk}' = G_{gk} (1-A_2)/A_2 = 0.3pF$ due to cathode follower bootstrapping
 - $C_{gp} = 3.8pF$ [6SN7 pin 4 grid]
 - $C_{gp}' = C_{gp} (1+A_2) = 7.2pF$ due to miller effect
 - Total loading capacitance $\sim 0.7+0.3+7.2 = 8.2pF$ (neglecting the step network)
 - RC corner frequency from $\sim 43k\Omega$ and $\sim 8.2pF$ is $\sim 450kHz$ max.
 - The 'new' amplifier [1] includes a shelf network across plate 47k, comprising (200pF and 4k7 Ω). Including the network was recommended if instability was experienced. The network steps down the loop gain from about 17kHz. [19] [20]
 - Stage gain at midband with feedback is $A_1' = 1.67$ (4.5 dB) = $\mu.R_3/(R_i' + R_3)$
 - $R_i' = R_3 \cdot (10.\mu/A_1 - 1) = 47k \times 11 = 517k$ ($A_1 \sim 16.7$)
 - Shelf start corner frequency $\sim 1/(2\pi.47k.200pF) = 17kHz$ (-3dB nominal corner frequency)
 - $R_i' \gg R_3$
 - R_i' will significantly reduce above nominal 17kHz. At high frequency above shelf stop corner f.
 - $R_3' = 47k/4k7 = 4.3k$
 - $A_1 = \mu.R_3'/(R_i + R_3') = 6.4$ (16.1dB)
 - $A_1' = A_1 / 10 = 0.64$ (-3.9dB) = $\mu.R_3'/(R_i'' + R_3')$
 - So a drop of -8.4dB from +4.5dB.
 - And $R_i'' = R_3' \cdot (10.\mu/A_1 - 1) = 4.3k \times 30 = 130k$
 - Shelf stop corner frequency $\sim 1/(2\pi.4k3.200pF) = 185kHz$ (-8dB flattening-out frequency)
 - Stop to start frequency ratio is 11:1.
 - Max phase increase of ~ 28 deg at about 3.3x start corner frequency $\sim 56kHz$, then dropping back to zero
 - The open-loop gain will start falling above 17kHz due to the shelf network at a max rate of $\sim -8dB/decade$, and level out above 185kHz.
 - The loop gain plot in Fig 2 of the 'improved' amplifier [1], shows the open-loop gain slowly falling from about 10kHz (as expected from the shelf network), although that fall then includes a contribution from the OT above about 40-50kHz, including a resonant dip around 80kHz.
- c) Driver stage RC roll-off due to effective output resistance and anode loading capacitance.
- $R_i \sim 9k\Omega$ (although cathode is unbypassed, there is no cathode voltage change)
 - $R = (R_i // R_{11} // R_{14}) + R_{15} = 7k + 1k = 8k$ [$R_{11}=47k$, $R_{14}=100k$, $R_{15}=1k$]
 - $C = C_g$ of output stage valve plus C_a of driver plus parasitics.
 - $C_a \sim 0.8-1.2pF$
 - $C_{gk} \sim 7pF$ { $\sim 6pF$ }
 - $C_g(a+s) \sim (1.1 + 3) \sim 4pF$ for KT66 { $\sim 3pF$ }
 - The grid to all except anode $\sim 14.5pF$ { $\sim 11pF$ }
 - $C_{ga} \sim 1.1pF$ { $0.2pF$ }
 - C grid to screen estimated at 3pF { $\sim 3pF$ }
 - grid to all other except screen and anode estimated at 7pF
 - Voltage gain $A_4 \sim 7$ {A515 results are ~ 6 }
 - $C \sim 1.2 + 7 + 7 \times 4 \sim 36pF$ { $\sim 25pF$ }
 - RC corner frequency from $\sim 8k\Omega$ and $\sim 36pF$ is $\sim 550kHz$ max {400kHz max}

- d) Although the phase splitter triode plate and cathode present different independent output resistances to the following stage, there is no high frequency imbalance as long as the following stage presents balanced loading (ie. no overdrive where grid conduction is not negligible). The output capacitance seen by each side of the splitter comprises the input capacitance from the driver stage, and also contribution from the splitter stage. A <1pF padder capacitance from driver 6SN7 pin 4 grid to anode may be needed to compensate for lower effective capacitance of that triode.

The phase splitter stage RC roll off is calculated from [4]:

- R' = effective plate or cathode load resistance [22k//470k=21k Ω]
 - R_i = 9k [6SN7 @ $I_p=5.2\text{mA}$, $E_b=110\text{V}$]
 - $R = (R' \cdot R_i / (\mu + 2)) / (R' + R_i / (\mu + 2)) = 401\Omega$ [$\mu=20$]
 - C_1 = differential output capacitance of phase splitter (considered to be $\ll C_2$)
 - C_2 = C_g of driver stage triode.
 - $C_{gk} = 3\text{pF}$
 - $C_{gp} = 3.8\text{pF}$ for 6SN7 pin 4 grid, and 4pF for other side
 - This imbalance may be trimmable
 - Triode gain of $\sim g_m \cdot R = 2.3\text{m} \times 7\text{k} = 16$
 - 6SN7 @ $I_p=5\text{mA}$, $E_b=215\text{V}$: $R_i \sim 9\text{k}$. $g_m \sim 2.3\text{ms}$
 - $R \sim R_i // 47\text{k} // 100\text{k} = 7\text{k}\Omega$
 - $C_g \sim 3 + 16 \times 4 \sim 67\text{pF}$
 - RC corner frequency from $\sim 400\Omega$ and $\sim 70\text{pF}$ is $\sim 5.7\text{MHz}$ max
- e) Input to first stage.
- This roll off is outside of feedback loop.
 - Grid stopper, or volume pot will introduce source resistance R
 - Contemporary volume pots were commonly from 250k to 1M Ω .
 - First stage triode grid capacitance
 - $C_{gk} = 2.6\text{pF}$
 - $C_{gp} = 3.8\text{pF}$ for 6SN7 pin 4 grid
 - Miller capacitance $\sim 14 \times 3.8 = 53\text{pF}$
 - RC corner frequency from 250k Ω and $\sim 56\text{pF}$ is $\sim 12\text{kHz}$.

5. Power Supply

The 'original' circuit used a Marconi U52 diode rectifier with directly heated cathode requiring 5V at 2.25A. The 'improved' circuit identified the more common 5V4 diode rectifier, with indirectly heated cathode that needs only a 2A heater current. The slower heat-up of the 5V4 indirectly heated cathode would have reduced the voltage stress on the filter capacitors, as the KT66's would be starting to load the supply at the time of power supply voltage rise. However, the 5V4 has a lower voltage rating than the U52, with some datasheets showing a 375VAC design max level, although the Sylvania datasheet shows design curves at 400VAC.

Almost all Williamson variants use a power transformer with HT voltage no more than 425-0-425V. The only commercial variant with a significantly higher HT voltage was the Heathkit W-5M with 465-0-465V. Higher voltage rated 5V 2A indirectly heated dual diodes include the GZ34 (introduced 1954) and the 5AR4 (introduced 1956-8) – see below for further assessment.

Contemporary parts can identify transformer and choke winding resistances. A Partridge TD2183 power transformer has primary 250VAC winding DCR=6Ω resistance and secondary 470V-0-470V winding DCR=91+96Ω resistance, with effective source resistance of about 120Ω. A Partridge TD2185 choke has 12H 200mA, and 158Ω DCR. A Partridge S15 choke has 30H 15mA, and 1.1kΩ DCR.

The PSUD2 simulation in Figure 5 shows a repetitive peak diode current of 0.5A which is just under the 5V4G max rating, and a hot turn-on causes a short-duration peak current of about 1A which is well under the max rating. The simulated hot turn on event indicates a ~2Hz ring on the output stage, and a slower damped response on the preamp stage rails, and an initial overshoot of nearly 600V. The simulation needs to be treated with caution as PSUD2 circuit loadings are modelled as either a constant current source or an end resistance, and PSUD2 is not being able to model non-linear choke inductance as DC current level changes.

CH1 and CH2 resistance provides substantial dampening to any transient disturbance. The PSUD2 simulation in Figure 6 shows a 5mA step change to the output stage loading, where some damped resonance is observable. For normal operation below clipping, the Williamson amp presents no transient loading.

Simulation shows that changing the diodes from valve to ss increases supply voltage rails by ~35VDC, but otherwise shows little effect to transient performance due to the well damped chokes.

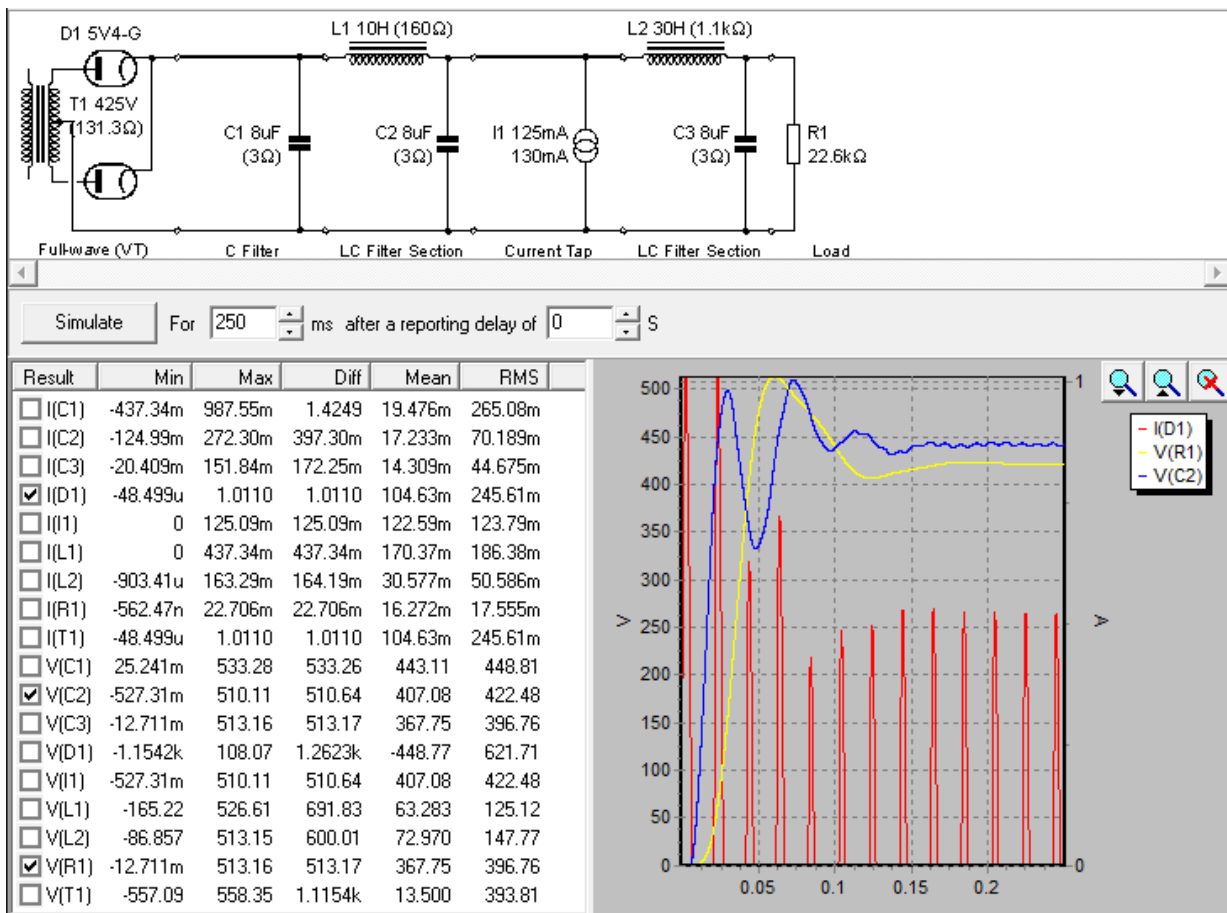


Figure 5. PSUD2 hot turn-on simulation result.

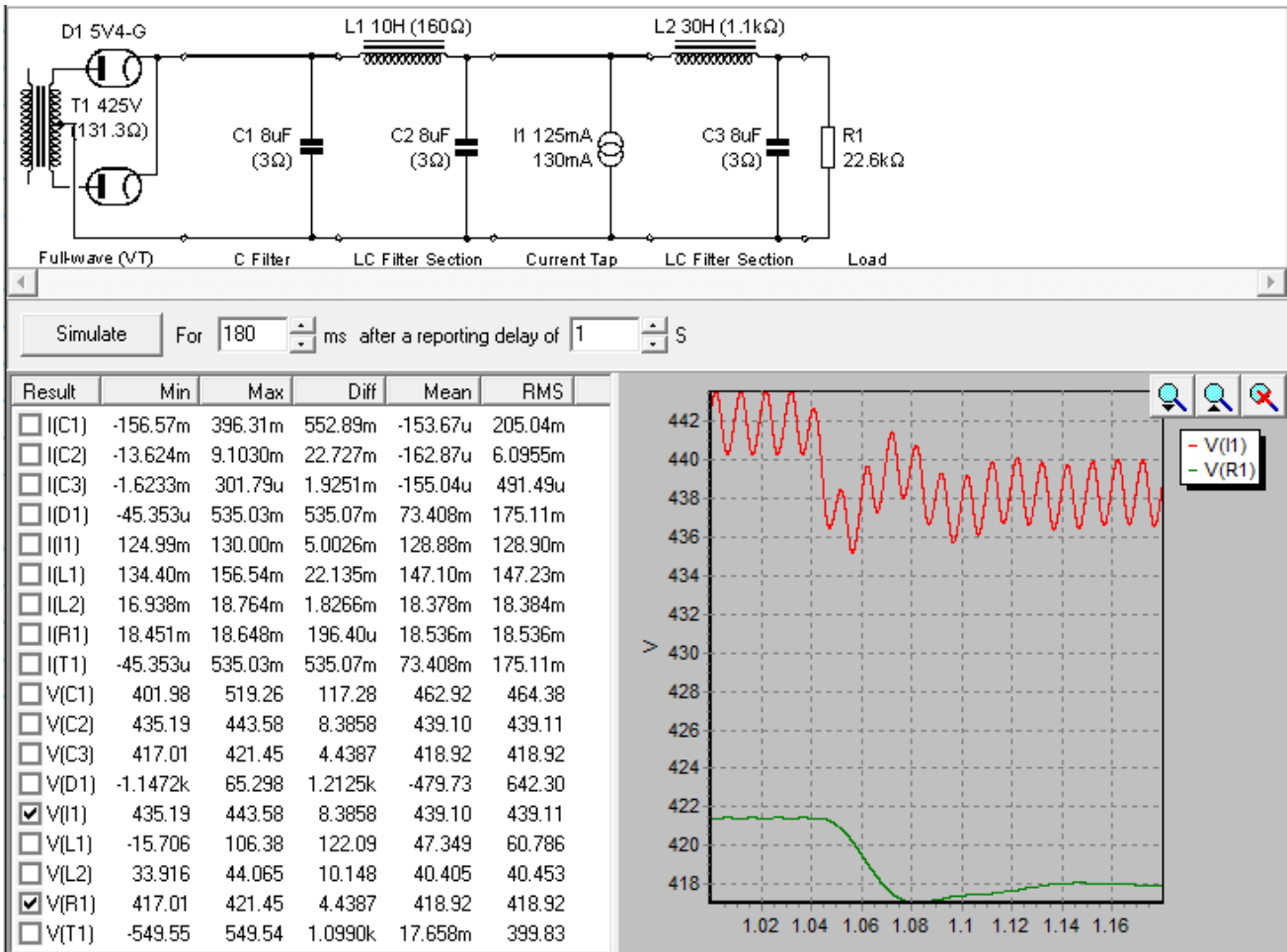


Figure 6. PSUD2 step load change simulation result.

The addition of power transformer secondary fuse protection is recommended. Simulation results in Table 1 for a fuse in the CT, and in Table 2 for a fuse in each winding arm, indicate an IEC 60127-2/3 quick acting F type fuse is appropriate [8]. Note that UL248-14 compliant fuses are not directly comparable.

| | | | |
|-------------------------------------|-------|-------|------------|
| Simulate period in PSUD2 | 10ms | 50ms | continuous |
| Simulated RMS current | 0.61A | 0.53A | 0.25A |
| Multiplier (for 0.315A fuse rating) | 1.9 | 1.7 | 0.8 |
| Multiplier (for 0.25A fuse rating) | 2.4 | 2.1 | 1.0 |
| IEC 60127-2 F min limit multiplier | 4 | 2.75 | 1 |

Table 1. CT fuse position assessment

| | | | |
|------------------------------------|-------|-------|------------|
| Simulate period in PSUD2 | 10ms | 50ms | continuous |
| Simulated RMS current | 0.61A | 0.41A | 0.18A |
| Multiplier (for 0.2A fuse rating) | 3.1 | 2.1 | 0.9 |
| IEC 60127-2 F min limit multiplier | 4 | 2.75 | 1 |

Table 2. Diode arm fuse position assessment

A 315mA F 250VAC fuse in the CT connection suitably keeps operating current below the minimum limit ratings of the fuse. For a fuse in each winding arm, a 200mA F 250VAC fuse is appropriate. The continuous rms current level at idle is effectively the worst-case condition, as power supply current will reduce with signal level. Even though the secondary winding voltage of 425Vac exceeds the nominal 250Vac fuse rating, a 250Vac rated fuse is acceptable in this secondary side application.

Although a mains primary fuse is shown, no fuse rating is given. The power transformer is about 150-200VA with about 105W of secondary loading, indicating that a 0.8-1A Slow Blow fuse for 230VAC supply should manage the transformer and heater in-rush current.

It is not appropriate to include fusing further in to the amplifier circuitry, due to the substantial resistance of any fault circuit path through an output transformer winding or power supply choke. In addition to appropriate fusing of the primary and secondary sides of the power transformer, adding two series UF4007 in series with each anode of the 5V4G reduces the risk of 5V4G failure [46], [47].





Two alternative diodes are compared to the 5V4G in Table 3. Comments on diode choice are:

- Partridge TD2183 has sufficient supply impedance to suit any diode in Table 3.
- The GZ34 and 5AR4 allow an increase in C9 capacitance, and additional PIV margin, but will raise the B+ supply voltage somewhat.

| | 5V4G | GZ34 | 5AR4 |
|------------------------------------|--------------|--------------|--------------|
| Heater supply requirement | 5V 2A | 5V 1.9A | 5V 1.9A |
| Peak Inverse Voltage, PIV | 1400 V | 1500 V | 1700 V |
| Peak continuous current, I_{ap} | 525 mA | 750 mA | 825 mA |
| Peak transient current, I_{apt} | 3.5 A | [3.0 A] | 3.7 A |
| Max AC voltage for capacitor input | 400V | 550V 400V | 600V 400V |
| Min plate supply resistance, R_t | 100 Ω | 100 Ω | 125 Ω |
| Max capacitor input capacitance | 8 μ F | 60 μ F | 40 μ F |
| Max DC output current | 175 mA | 250 mA | 250 mA |
| Plate voltage drop at 175mA | ~ 25V | ~ 13V | ~ 13V |

Table 3. Diode option assessment

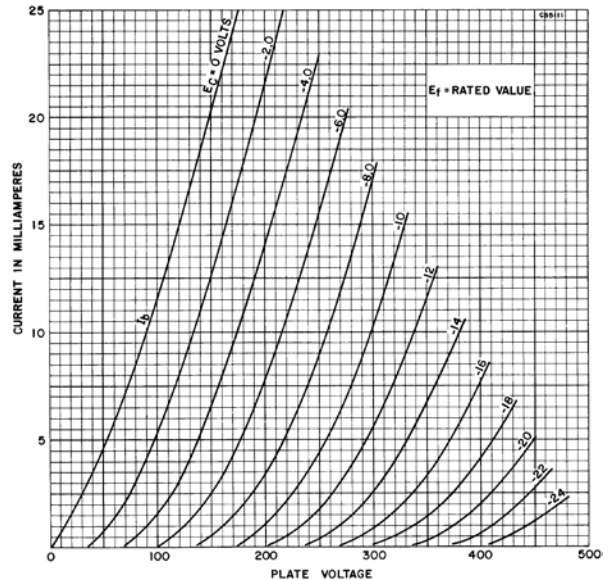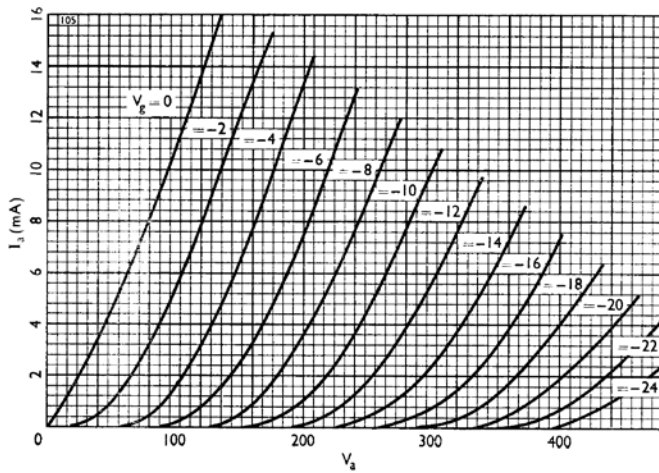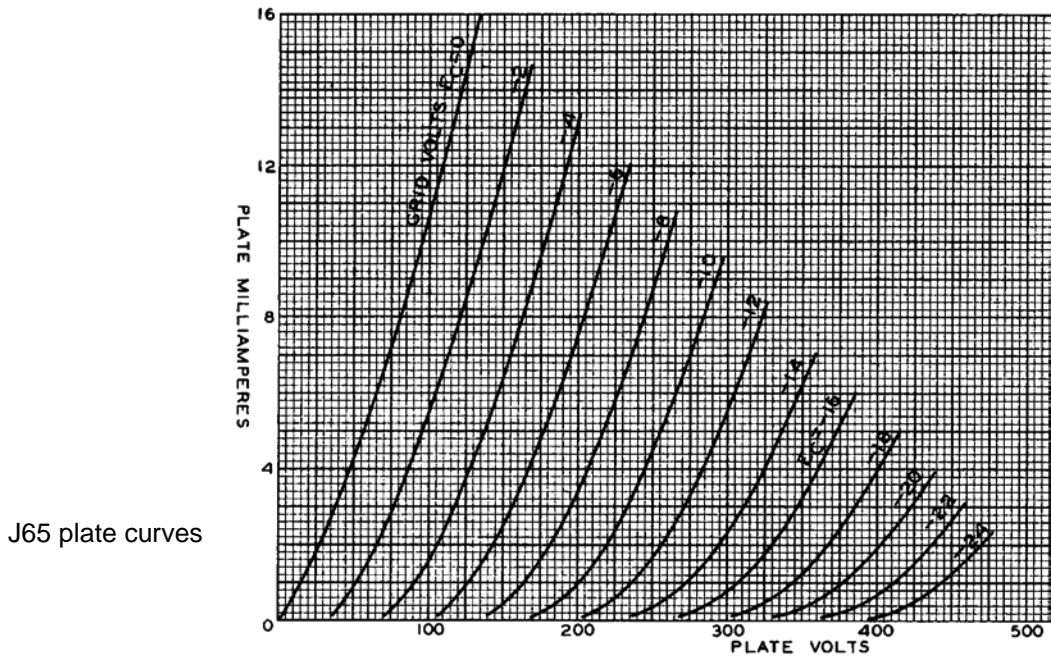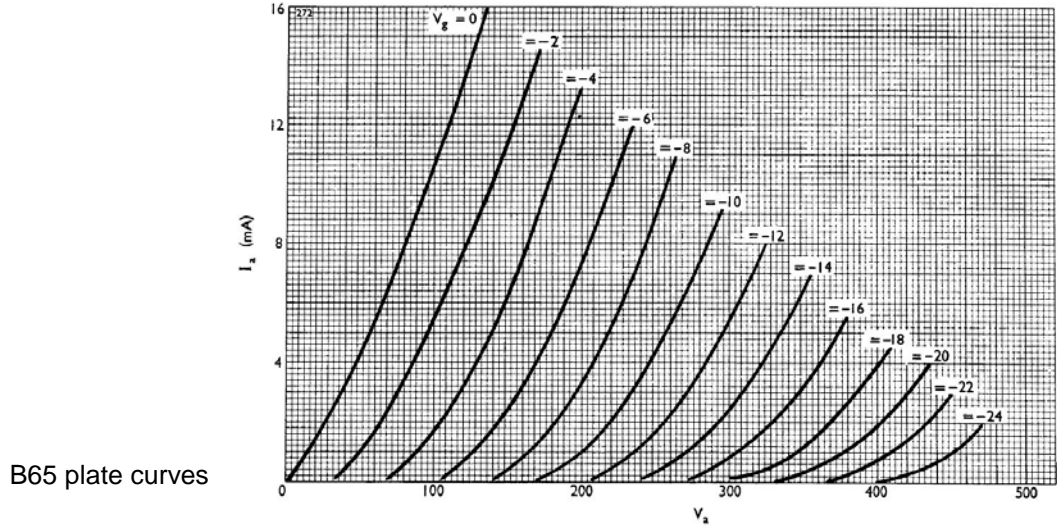6. Signal stage valve types and bias conditions



L63 plate curves

6SN7 plate curves

Figure 7. L63, 6J5 and 6SN7 comparison

Williamson appears to have originally used Marconi L63 single-triode valves in the amplifier's development in the early-mid 1940's, and then indicated that 6SN7 dual-triode valves were an alternative in the late 1940's. Figure 7 indicates that the L63, 6J5, B65 and 6SN7 have the same plate characteristic curves. The L63 triode and B65 dual triode have slightly higher grid to cathode and grid to anode capacitances than a 6SN7 dual triode, but the total heater requirement is the same. Figure 8 to Figure 10 show the loadline and idle bias point for each stage in red using just the 6SN7 curves.

In 1961, Wright [9] described changes to the bias points of the first, phase splitter and driver stages, and provided measured results on intermodulation distortion that indicated a significant improvement, although results were in general sparse and subjectively presented. Wright makes the ambiguous assertion that the US 6SN7 does not work well in the Williamson design, however a quick review of US 6SN7 datasheets and the Marconi L63 or 6J5 show no difference in plate characteristics! In summary, Wright's changes are:

- First stage – increase bias voltage from ~2.1V to ~3.0V, and maintain anode voltage at ~100V.
 - R2: 33k Ω → 47k Ω , R4: 470 Ω → 910 Ω
 - Supply voltage falls from ~305V to ~250V.
 - Idle current falls from ~4.5mA to ~3.25mA
 - Changing R4 requires a feedback network change. An alternative is to retain the 470 Ω as the feedback point, but insert another bypassed 470 Ω in between the 470 Ω feedback point and the cathode – the bypass would need to be circa 470 μ F to maintain a corner frequency below 1Hz.
 - 6SN7 @ $I_p=3.25\text{mA}$, $E_b=100\text{V}$: $R_i\sim 9.2\text{k}$, $g_m\sim 2.2\text{ms}$, $\mu=20$ {likely minor changes}
 - Stage gain $A_1 = V_{o1} / V_{gk}$
 $= \mu.R_3 / (R_i + R_3) = 16.7$ {no change}
 - Gain with R4 signal bypassed to ground
 - Stage gain $A_1' = V_{o1} / V_{in} = A_1 / 10 = 1.67$ (4.5 dB) = $\mu.R_3 / (R_i' + R_3)$
 - Gain with 20dB feedback connected
 - Hence $R_i' = R_3 \cdot (10.\mu/A_1 - 1) = 11 \times 47\text{k} = 517\text{k}$ {no change}
 - Stage gain $A_1'' = V_{o1} / V_{in}$ (R25 disconnected, and not grounded)
 $= \mu.R_3 / (R_3 + R_i + (\mu+1).R_4) = 20 \times 47\text{k} / (47\text{k} + 9\text{k} + 21 \times 910)$
 $= 940\text{k} / 75\text{k} = 14.3$ (22dB) {was 23dB}
 - V_{in} includes voltage across R4, but no feedback from output
 - eg. low or high frequency operation
 - $R_i'' \sim R_i + (\mu+1).R_4 = 9.2\text{k} + 19.1\text{k} = 28.3\text{k}$ {was 19.1k}
 - Quasi-open-loop circuit configuration
- Phase splitter stage – increase supply voltage from 325V to 410V, and maintain anode current at ~5mA to increase idle V_{ak} from ~110V to ~190V.
 - R6: 22k Ω → 3k9 Ω .
 - Bias voltage increases from ~2.2V to ~6.2V.
- Driver stage – increase plate voltage from 160V to 230V, with V_{gk} increased from 4.5V to 8.5V.
 - R10: 390 Ω → 1k Ω .
 - Stage current reduced from ~11mA to ~9mA.

Some comments can be made about these changes:

- Each of the modified stages has an increased signal swing capability that could reduce gross distortion at high signal levels if those stages were starting to limit signal swing.
 - For mid-band signals, only the driver stage approaches its voltage swing limits, and driver stage low order harmonic distortion is slightly higher with the Wright change.
 - For low/high frequency signals, the first stage gain increases significantly, and depending on the coupling corner frequencies, the driver and output stages will see much higher levels due to their gain.

- The idle current requirements are not changed significantly, nor are the valve operating parameters of μ , g_m or R_i . The first stage gain is only marginally reduced. The phase splitter stage cathode voltage doesn't change. The driver stage change is independent of the changes made to the input and phase splitter stages. Stage gain changes to be confirmed by test.
- The operating currents of the first stage and phase splitter stage are now significantly different, which may affect the original low-frequency compensation from the cascaded stages.
- The very low frequency response may change below the C1, C2 decoupling cap corner frequencies.
- Increasing the driver stage common cathode resistance should marginally improve gain matching of the two triodes.

Figure 8. First Stage

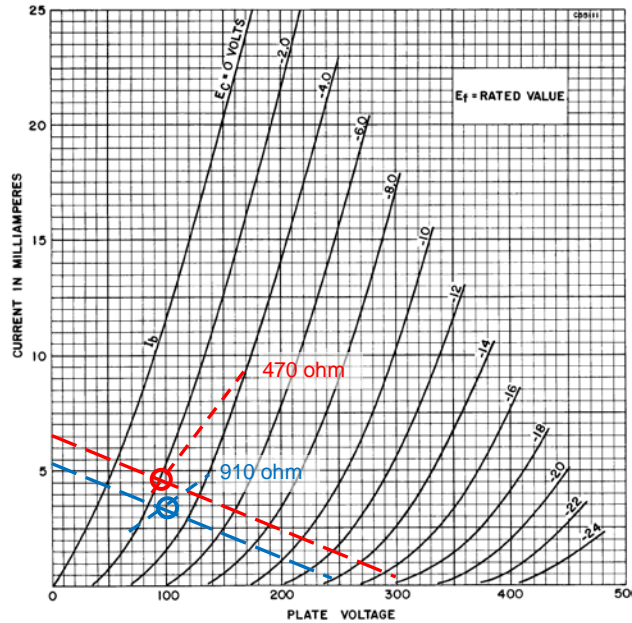


Figure 9. Phase Splitter Stage


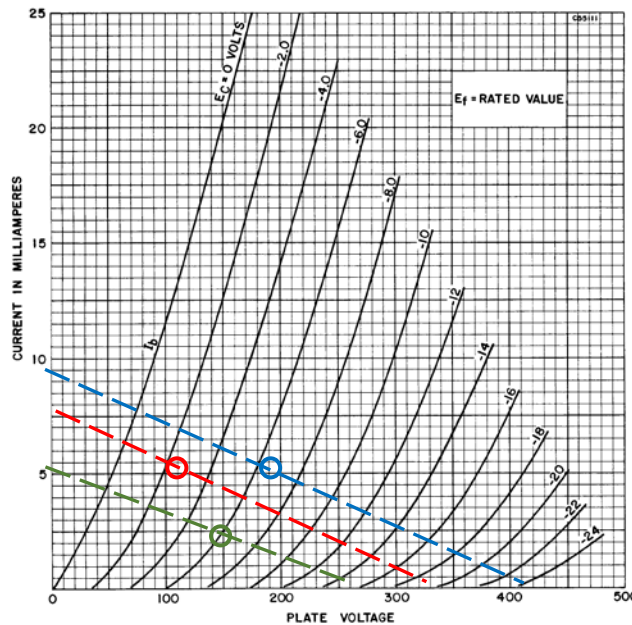


Figure 10. Driver Stage

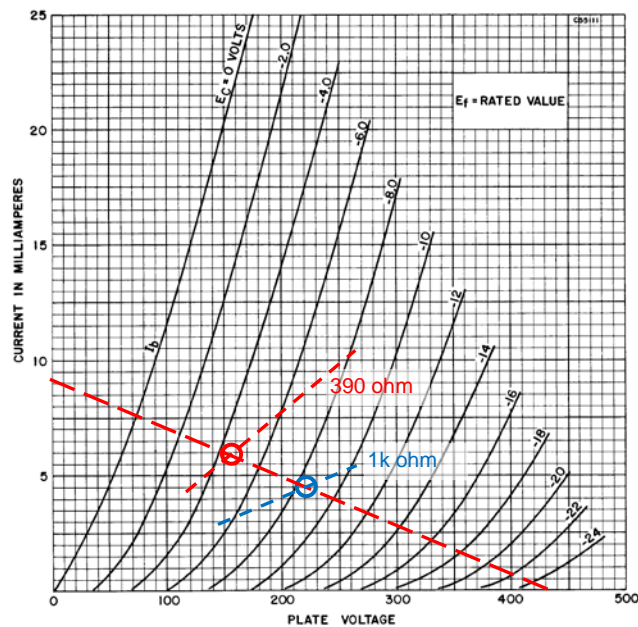

The 6CG7 / 6FQ7 is the novel equivalent to the 6SN7 octal. The 6CG7 typically has an electrostatic shield between plates, whereas the 6FQ7 does not.

The 12AU7 has commonly been used as a novel alternative to the 6SN7, given that it has similar μ , anode impedance, and lower capacitances, and the benefit of half the heater current requirement. Bernard compared distortion levels of 6SN7 and 12AU7 in 1953 [34]. Barbour presents historical details on the 6SN7, along with harmonic test results, however the test circuit and signal level conditions are not given [36] so the reported results may not relate to signal conditions in the Williamson. Morgan Jones [23] compared distortion levels for 6SN7 and 12AU7 in a μ -follower circuit at moderately high signal voltage levels (20Vrms), which indicate the 12AU7 has significantly higher harmonic levels, whereas the blackened glass 6SN7 has lower levels. My testing of thirteen 6SN7 and five 12AU7 as the driver stage valve in the same Williamson amplifier indicated the 12AU7 had typically more than twice the dominant second harmonic distortion than 6SN7.

7. Output stage bias conditions

Williamson's intent was to operate V5-V6 at max design rated dissipation level, to maximise plate voltage swing under class A operation of the output stage. The output stage operates a KT66 triode at an idle point of ~400V and 62mA (25W). A 10k Ω PP class A load represents a 5k Ω loadline. The idle grid bias is about -38V. The maximum voltage swing is about 275Vpk, or 390Vrms PP, with close to symmetric swing to grid conduction or cut-off operation. The turns ratio PP 10k:8.5 is 34:1, so max design output voltage is 11.5Vrms, or 15.7W.

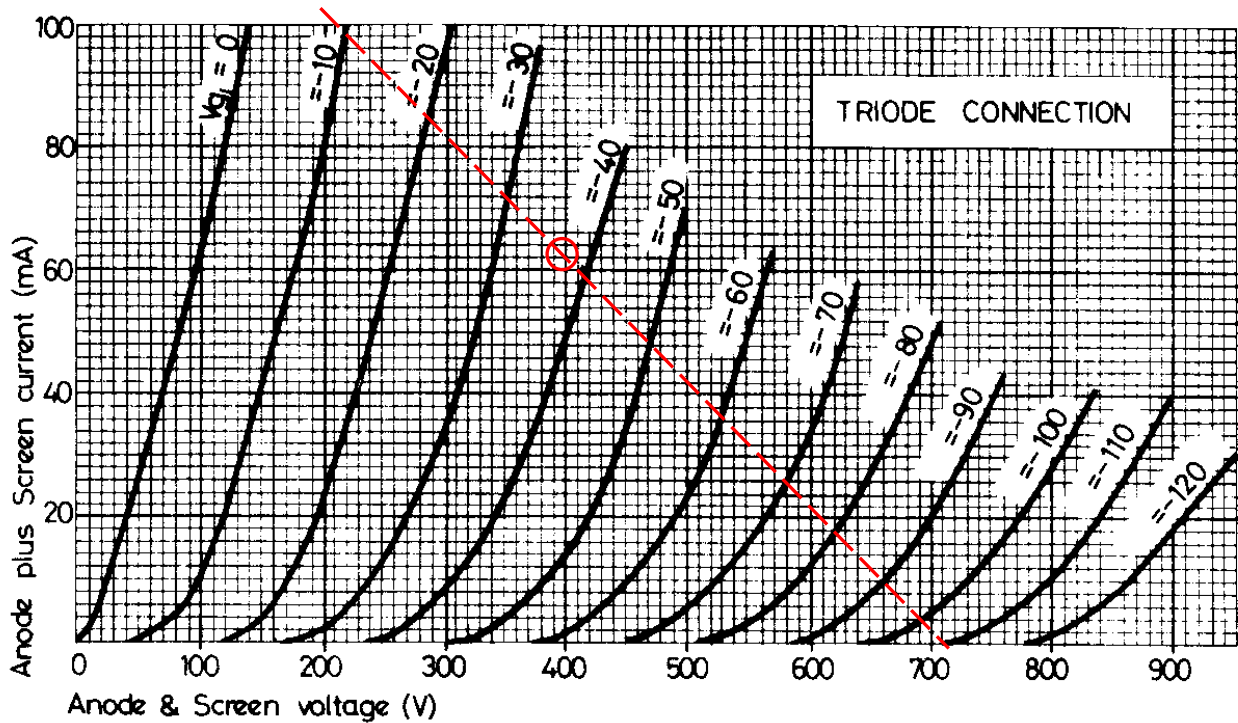


Figure 11. KT66 triode characteristics.

The output stage operates an 807 at an idle point of ~425V and 55mA (25W) ¹. A 10kΩ PP class A load represents a 5kΩ loadline. The maximum voltage swing is a bit lower at about 225Vpk to grid-conduction. The 807 was not originally rated for screen operation at 400V, but was subsequently re-rated.

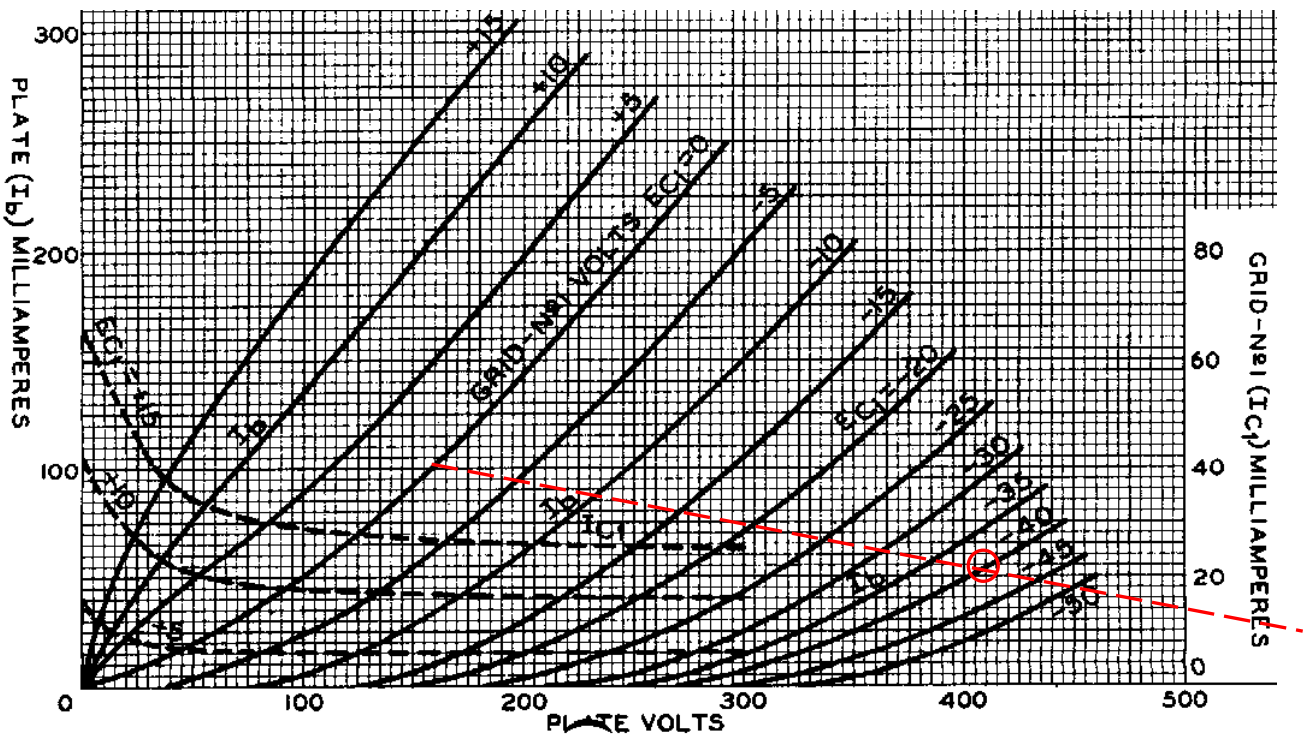


Figure 12. 807 triode characteristics.

¹ The Radiotronics A515 [2] operated each 807 at 400V and 59mA anode current at idle.

The RCA 6L6 beam pentode became more common than MOV's KT66, and RCA improvements out to the 6L6GC provide up to 30W plate dissipation, and 450V screen ratings. This allows a 6L6GC to operate at 80% plate power with the same bias current level as the KT66 at 100% plate power, for a longer service life.

The balance between the two valves in the output stage has a significant effect on low-frequency distortion, as the symmetry of flux swing in the output transformer core, and the inductance drop-off due to a DC bias [40], become more important. Tube rolling and static bias adjustment may change distortion performance markedly. Figure 13 is from the Heathkit W-5M instruction manual [10], with the x-axis representing a static bias current difference of $0.1V/30\Omega = 3.4mA$ (or 3% of 62mA) per division away from balanced 0V, and so a net DC current of 3.4mA. Different output transformers may vary with their inductance roll-off with DC bias.

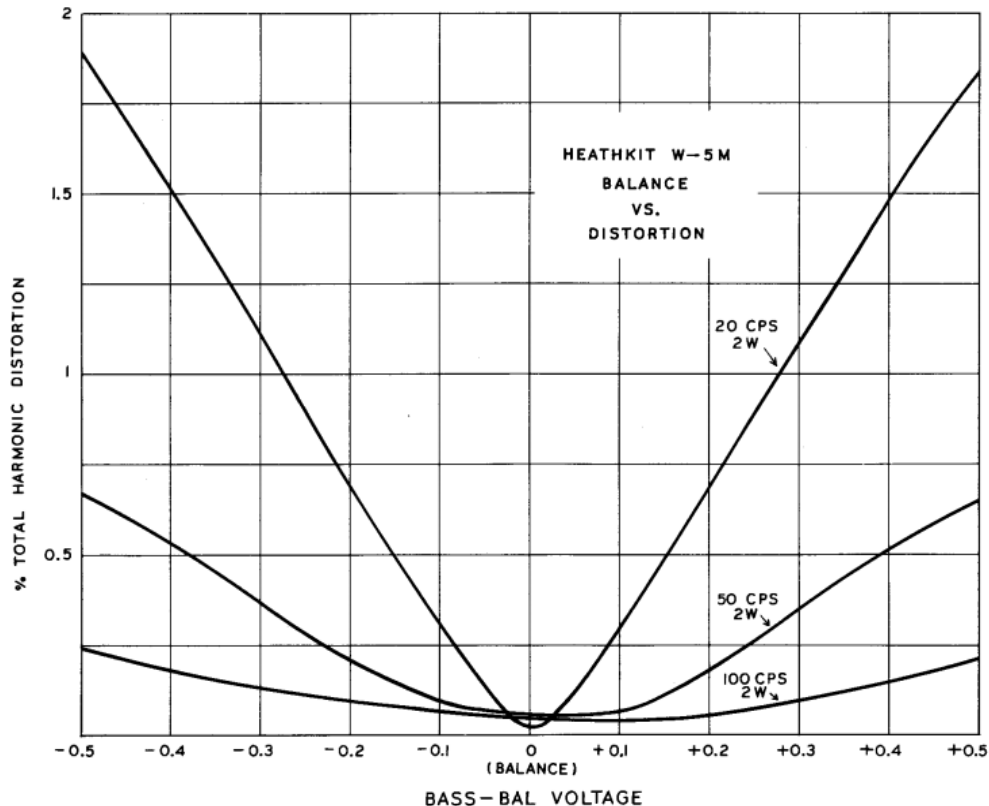


Figure 13. Output stage balance effect on low frequency distortion

The output stage was not normally operated with the valves in beam tetrode mode. The following comments apply to that mode:

- Grid characteristic curves not as linear as triode mode.
- Higher output stage gain.
- Screen current still included in common cathode voltage signal, but not in output signal.
- Screen voltage regulation influences gain.
- Lower miller capacitance due to decoupled screen.
- A beam tetrode has a higher R_a internal resistance
 - KT66 has $R_a \sim 22.5k$
 - 807 has $R_a \sim 30k\Omega$ (24k at 300V, 39k at 500V)
 - the output stage PP R-C high frequency roll off is likely to reduce by about $1.45k\Omega/30k\Omega \sim 5\%$. A triode KT66 has a closed loop roll-off of $\sim 300kHz$, and an 807 regulated screen has a closed loop roll-off of $\sim 60-70kHz$.
 - reduces speaker output damping factor
 - increases the low frequency RL to become the dominant pole.
- Output stage B+ can be increased beyond $\sim 440V$, as screen voltage is held lower.
- The 807 pentode curves for V_{g2} regulated at 300V in Figure 14 show the idle cathode voltage bias is lower (approx. -34V), and that voltage swing to grid-conduction is increased to about 370Vpk, although linear operation would significantly degrade beyond about 300Vpk. The STC application report extract below indicates lower cathode bias voltage (perhaps as $V_{g2} = \text{Screen voltage} - \text{bias}$).

The June 1954 STC 807 application report provides results for 807 in pentode mode in class A PP, with the 807's idle anode dissipation at 24W.

Class 'A' Amplifier (Push-Pull):

TETRODE CONNECTION:

| | | | | | | | | |
|-------------------------------------|------|-------|------|------|------|--------|--------|-------|
| Plate Voltage | 250 | 270 | 270 | 500 | 500 | 600 | 600 | volts |
| Screen Voltage | 250 | 270 | 270 | 300 | 300 | 300 | 300 | volts |
| Grid Voltage | -16 | -17.5 | — | -27 | — | -29.5 | — | volts |
| Autobias Resistor | — | — | 125 | — | 270 | — | 360 | ohms |
| Peak AF Grid-Grid Voltage | 32 | 35 | 40 | 54 | 72 | 59 | 81 | volts |
| Plate Current (no signal) | 120 | 134 | 134 | 100 | 100 | 80 | 80 | mA |
| Plate Current (max. signal) | 140 | 155 | 145 | 154 | 119 | 150 | 97 | mA |
| Screen Current (no signal) | 10 | 11 | 11 | 2.5 | 2.5 | 1.5 | 1.5 | mA |
| Screen Current (max. signal) | 16 | 17 | 17 | 20 | 16.5 | 17.5 | 17.5 | mA |
| Output Load Impedance (plate-plate) | 5000 | 5000 | 5000 | 8000 | 9000 | 10,000 | 10,000 | ohms |
| Total Harmonic Distortion | 2 | 2 | 4 | 2.6 | 2.7 | 2.2 | 4.1 | % |
| Power Output | 14.5 | 17.5 | 18.5 | 38 | 32.5 | 47.5 | 36.5 | watts |

-Values are given for two valves.

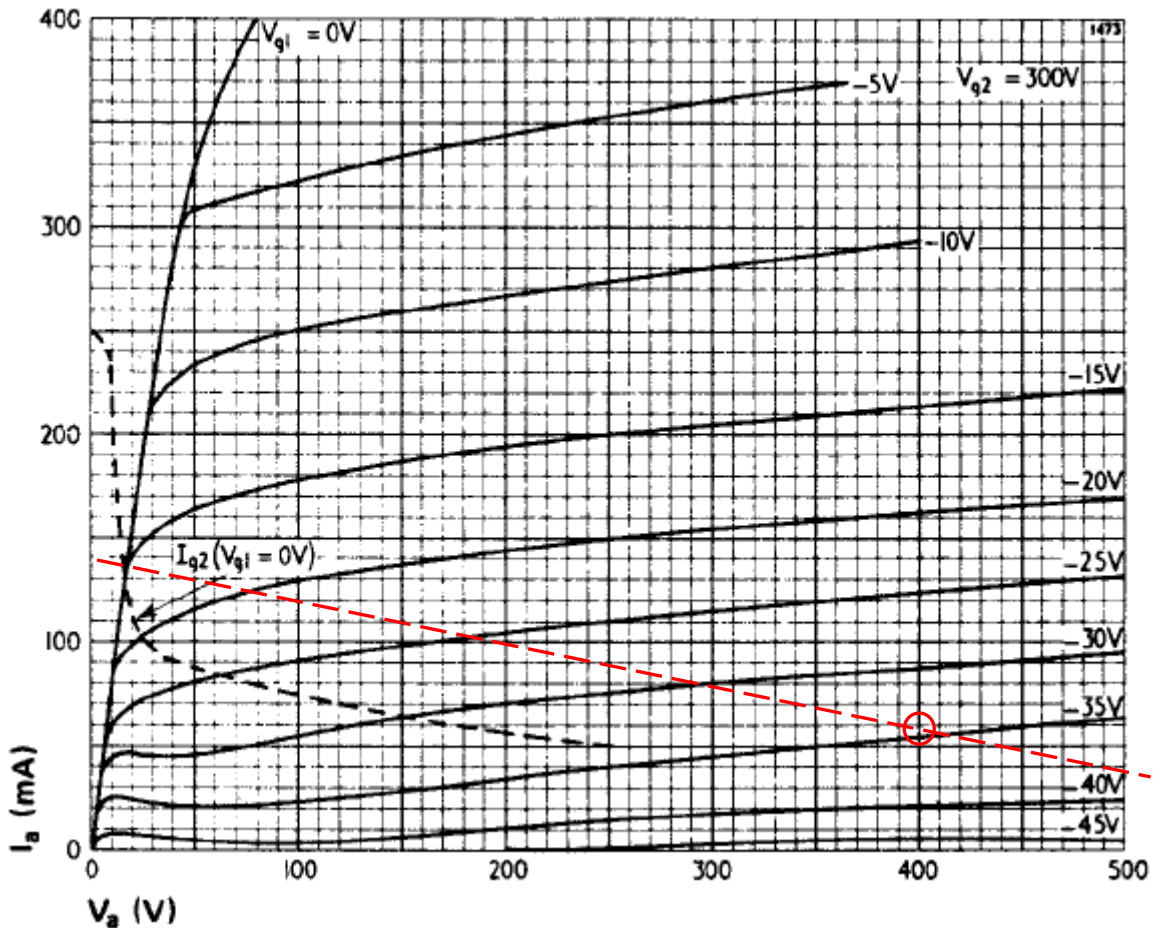


Figure 14. 807 pentode characteristics for 300V screen and 10kΩ PP loadline.

8. Changes

The original Williamson amplifier circuit was developed and demonstrated mainly in 1944, with the 1947 WW article written in late 1944 as preparation for an audio presentation to the Marconi-Osram Board [43]. The 'new' circuit from WW 1949 only had the high frequency shelf circuit added to the input stage, and alternative valves identified, with the articles mainly adding preamplifier and tuner designs, and practical advice to cover reader feedback.

The following is a list of changes known to have been made to the Williamson circuit, with reference to the first use of the change, and any relevant comments. Some changes are practical and appropriate to improve performance, and make the amp bullet proof, although further assessment and testing may well be required.

- a) Including an adjustment pot in the driver stage to adjust imbalance.
 - Williamson originally included a 25k Ω adjustment pot in the common supply rail for the driver stage to allow adjustment of gain symmetry of each driver and output stage cascade circuit. The pot was removed in the 1949 'improved' circuit (with benefits of lower parts count and increased reliability, and safer operation given the pot was at B+) based on only minor variation in performance using typical valves and matched parts.
 - Nowadays, a pot may be useful to allow distortion minimisation, given the typical use of aged parts and the ease of distortion measurement.
 - To maintain reliable and safe operation, inserting a 20k Ω multiturn 0.75W trimpot in each anode load leg (with wiper connected to one end for fail safe operation) is appropriate. Modern 19mm trimpots have a 0.75W rating, and an insulation rating of about 1kVDC.
 - Tube rolling can show up distortion performance changes.
 - [Varying the heater power](#) of output stage valves can adjust their balance.
- b) Adding an output stage cathode bypass capacitor to lower distortion.
 - First referenced in Dec 1950 [11]. Claimed reduction in distortion at higher output signal levels.
 - Kiebert [44] in April 1955 measured lowest IM when bypass capacitor was at a particular tapping of the cathode bias resistance.
 - A contemporary assessment by Mitchell [39] in Nov 1955 used the UTC W-10 Williamson amplifier to measure THD and IM with/without a bypass capacitor for KT66, 5881, and 1614 output valves, and for varying degrees of circuit unbalance. In general, results showed that THD could rise or fall, depending on the valve. CCIF IM results in general showed a slight improvement at higher output power levels with the bypass capacitor.
 - Author measured THD for sample Williamson with feedback removed for (a) standard output stage, (b) capacitor bypass, and (c) CCS (LM317) in cathode. THD was the same for all options, except that standard circuit had lower THD below about 9W.
 - During max output and overload conditions, the cathode voltage generally falls, so there is no benefit in deploying circuitry such as a Paul Ruby zener clipper (or simpler zener plus steering diodes) on the output stage coupling CR nodes [32].
 - Author measured significant reduction in harmonic and intermodulation distortion in an 807 pentode mode output stage Williamson by adding bypass capacitor.
- c) Modifying the CR coupling network corner frequencies for better low frequency response.
 - First referenced in Feb 1952 [12]. Subsequently the change was typically to increase C3, C4 from 50nF to 250nF.
 - Phase splitter stage CR coupling frequency lowered (from 6.8Hz to 1.4Hz) to separate it from the now dominant driver stage pole frequency.
 - The Heathkit W-5M [10] halved the phase splitter corner frequency (100nF), and quartered the driver stage corner frequency (1 μ F) to both separate the stage corner frequencies and lower them relative to the output transformer roll-off.
 - Raising the driver stage output coupling cap values may adversely degrade recovery from any transient blocking distortion event occurring from output stage grid conduction.

- The nominal OT corner frequency is ~6.4Hz for UL mode KT66, assuming 100H, and so becomes the highest corner frequency.
- Driver stage CR coupling frequency negated by paralleling C6, C7 with high value resistance.
 - First referenced in Nov 1955 [13].
 - The change used a parallel 470k-1M Ω , with a zero corner frequency ~0.63Hz (~ a decade below pole frequency), to improve phase margin.
 - The added resistor changes the output stage bias level, which needs to be readjusted. Also there is risk introduced that removal or failure of V3 or V4 would lower V5/V6 bias leading to red-plating/damage. Increasing the parallel resistor by up to about 3x should still provide some phase margin benefit and alleviate bias shift.
- Phase splitter stage output CR step/shelving network.
 - Additional parallel Cx-Rx network in series with output coupling C (C3,C4), as detailed by Roddam [20] in 1951, with examples including Partridge (1947), and GEC [38] in 1957. Similar very low DC frequency pole response, but as coupling C impedance falls then a shelf attenuation is introduced by Rx and the driver stage grid leak. Then at higher frequency, Rx is bypassed by Cx, and normal mid-band gain is attained.
 - Similar to the first-stage HF shelf network, the aim is to reduce open-loop gain once outside of the nominal audio band, but still within the amplifiers bandwidth, so that stability margin is improved at the ends of the amplifier bandwidth, and to reduce the likelihood of overdriving the output stage in to grid-conduction from low frequency transients. The aim is for the shelf attenuation to at least offset the gain peak (typically around +4 to +6dB at 2-3Hz), so for the design parameters in [19] then at least n=2 (-9dB shelf), up to about n=5 (-15dB shelf) as typically used by Patrick Turner in his amps to improve LF stability margin [37].
 - With a 250nF coupling cap C, and 470k driver stage grid-leak R, and a 10:1 ratio of C:Cx, and 2.1:1 ratio of Rx:R (where Rx=1M Ω , and Cx = 27nF), the shelf attenuation has a mid-frequency of about 10Hz (27nF-470k Ω), with attenuation starting about $3 \times 10 = 30$ Hz, and plateauing at ~ -9dB at about $0.3 \times 10 = 3$ Hz [19]. Phase shift will start falling to -10deg at about $6 \times 10 = 60$ Hz, and fall to a minimum of about -30 deg at ~10Hz, and then rise back to about -10 deg at $0.15 \times 10 = 1.5$ Hz. The final low pass filter response from C and Rx has a 0.6Hz corner, with a minor influence on phase shift at about 2Hz.
 - Similar shelving response achieved by using a series RC network in parallel with a C, as used by Kiebert [44].

d) Altering the feedback

- Including a phase lead filter (capacitor in parallel with R25) was first referenced in Feb 1952 [12].
 - Used to provide some 'free' phase margin improvement by placing corner frequency sufficiently above both the gain margin and phase margin frequencies, and to not degrade stability margin for no load or capacitive load conditions. 30 degree advance shift is provided at 60% of the RC corner frequency.
- Lowering the feedback level from 20dB when stability margin improvement is needed.
 - The Heathkit W-5M used 18.1dB feedback and suggested that could be lowered should the stability be marginal.
- Including additional output to driver feedback loop
 - Marshall [35] describes a circuit using a centre-tapped speaker output to provide feedback direct to the driver stage cathodes. No use of this technique has been identified in the literature so far. The typical interleaved secondary windings can usually be configured to allow a CT connection to ground, although that would likely restrict the speaker impedance options.
- Including an additional inner feedback loop.
 - Hafler [22] introduced a 100pF capacitor from driver V4 anode to R4 to achieve additional 12dB margin, with bandwidth reduced from 200kHz to 80kHz and some minor increase in 20kHz distortion. The added capacitor imbalances the driver stage output, and lowers the driver stage RC roll-off from ~550kHz to ~170kHz.

- A padding capacitor was not added to the other driver anode.
 - Duerdoth patented a subsidiary feedback technique circa 1950 that applies local feedback around the first stage(s) that is frequency restricted to outside the main signal bandwidth, such that the amplifier roll-off beyond the main bandwidth has a slower roll off [28], [29]. The technique requires the first stage(s) to have a very wide bandwidth, and the feedback signal is filtered for appropriate frequency response.
 - This technique appears to be what Hafler has introduced. The driver stage is used for feedback take-off, as the closed loop gain of first stage and phase splitter is only ~ 1.5, whereas the driver stage signal has a gain $A_1 \cdot A_2 \cdot A_3 = 21$. Also, loading the first stage anode would likely lower its corner frequency too much.
 - The first stage has a roll-off ~370kHz, which would likely work with an inner loop feedback corner of 230kHz to provide a subsidiary loop response described by Duerdoth, but not specifically using the patented means.
 - Although not applied to the Williamson amp, Kauder [49] applies feedback from an output stage anode to the global feedback point to control the high frequency peak in a very similar amp circuit.
- e) Altering the output stage from triode PP, to 'ultra-linear' PP.
- First referenced in June 1952 [14]. Within 3 months, Williamson responded with an article [15] in Wireless World with co-author Walker from 'QUAD', concluding that QUAD's use of an output stage cathode feedback winding was a better outcome than the UL screen feedback tapping.
 - The internal resistance of a beam pentode in UL configuration is higher than in triode mode.
 - KT66 increases from 1.45k to 3.1k at 20% impedance tap [21].
 - For low frequency response, UL mode increases RL corner frequency from 3.9Hz to 6.4Hz, which may degrade low frequency stability margins.
 - For high frequency response, UL mode would significantly lower $B = X_c/R_i$, and R_o/R_i . The net result should reduce response peakiness, especially for no load conditions, along with some minor reduction in -3dB frequency.
 - The driver stage RC roll-off frequency should increase due to lower V5-V6 miller capacitance.
- f) Fixed bias instead of cathode bias
- Not a practical option for Williamson, as selenium diodes only became available in the late 1940's.
 - Sparsen & Sprinkle 'Maestro' 1952 amp used fixed bias.
 - Hust in 1953 used fixed bias.
 - Hafler in 1956 article [22] on modernising the Williamson.
 - Easy technique to balance output stage bias currents, and removes need for power pots.
 - A lower B+ level (~40V) can be operated.
 - Max grid leak resistance needs to be lowered from 500k to 100k, but Williamson circuit uses 100k.
- g) DC elevation of heater supply.
- First referenced in Feb 1952 [12].
 - Reduces maximum heater-cathode voltage V_{k-h} for 6SN7 (datasheet recommended limit of 200V).
 - Phase splitter cathode has $V_{k-h} \sim +100V$, plus a minor level of signal voltage swing.
 - Reduces heater-cathode resistive AC hum transfer when $|V_{k-h}| > \sim 20V$.
 - Elevated supply ~ +40Vdc (from a divider, or output stage cathode bypass capacitor if used)
 - $V_1 V_{k-h} \sim -38V$; $V_2 V_{k-h} \sim +60V$; $V_{3,4} V_{k-h} \sim -36V$
- h) Humdinger pot to minimise heater hum from residual AC coupling to grids.
- First referenced in Nov 1955 [16].

- Setup should be done open-loop, as closed loop feedback will attenuate the hum level.
- i) Modifying bias points of V1, V2, V3, V4 to improve signal swing headroom.
- Pilot Radio's Pilotone AA-901 model from 1952 modified the bias settings for V1 and V2.
 - V1 bias voltage was lowered to 1.1V by reducing the supply rail from 305V to 185V. The anode voltage is lowered to 50V, from 100V, to adjust bias for the phase splitter. Given the low gain from the input stage, this appears to have a negligible negative effect.
 - V2 bias is increased to 6.0V by reducing supply rail from 325V to 261V, and increasing arm resistance from 22k to 27k – see Figure 9. The higher bias may help avoid stage clipping.
 - Referenced in June 1961 [9]. See section 6.
- j) Care with component selection, matching, and layout.
- Williamson indicated that certain layout aspects were significant:
 - Coupling between output transformer and the power transformer and first choke can degrade hum level.
 - High level and output level signal cables should be well separated from input wiring. An under-chassis metal screen between V1-2 and V5-6 was recommended to isolate V5-6 anode/screen voltages.
 - Stray coupling capacitance from wiring and parts to either ground, or other circuitry, can noticeably affect high frequency roll-off, especially for the first stage and driver stage.
 - Coupling caps C3, C4, C6, C7 should not be placed on or near the chassis or other wiring, and the outer foil end should connect to the anode side of circuitry.
 - Kiebert was the first reference in Aug 1952 [17] to highlight the need for careful parts selection so as not to degrade distortion or noise performance.
 - The original parts list used mainly $\frac{1}{4}$, $\frac{1}{2}$, and 1W carbon composition resistors. Vintage CC resistors all typically drift $> +20\%$ over the decades, especially if they have DC voltage across them. Modern metal oxide 2W resistors are small, low noise, and stable with 500V rating.
 - Ready access to resistance and capacitance meters, and 1% tolerance resistors, can now achieve excellent matching.
 - Free PC distortion measurement software can be used to minimise harmonic and intermodulation distortion, when feedback is disconnected, by tube rolling in all stages (eg. to match driver and output stage dynamic balance). A typical simple soundcard allows distortion assessment to well below 0.01%, and noise floor confirmation to $< 90\text{dB}$ below rated output.
 - The input, phase splitter and driver stages could use 12AU7 with no need for any circuitry changes, except for the valve holder and heater. An example is the Heathkit W-5M. However harmonic distortion is likely to be higher, especially for a 12AU7 in the driver stage which operates at higher signal levels – see section 6.
 - Kiebert (1952) recommended changing the first 6SN7 for a 12AY7 to lower hum, however that result may have been achieved by using an elevated heater or as a result of circuit resistor changes needed due to significantly different parameters. Kiebert later (1955) identified high IM from the 12AY7 in phase splitter stage.
 - Kiebert recommended changing the driver stage 6SN7 for a 5687 due to better triode matching. The 5687 has significantly different parameters and needs circuit resistor changes.
 - Parallel each driver stage grid leak resistor (R8, R9) with 100pF to lower inter-stage RC corner frequency from $\sim 5\text{MHz}$ to $\sim 2\text{MHz}$. The added capacitance dominates the driver stage capacitances [23], but need to be matched to maintain high frequency symmetric loading on the PI stage.
- k) Increasing power supply decoupling values.
- The value of C9 can't be increased due to rectifier peak continuous current limits (see 5). Changing the rectifier type may allow an increase in C9 (see 5).
 - Increasing C8 from 8u to 22u dampens any ringing on the output stage rail due to a step load change, but also increases the hot turn-on overshoot and diode peak current levels by a small amount.

- Increasing C5 as well to 22u dampens any ringing on the driver rail supply.
- Increasing C1, C2 power supply decoupling cap values lowers the corner frequency of the decoupling zeroes. Increasing C1 may reduce the phase shift benefit on low frequency stability margin. Increasing C2 would reduce phase splitter asymmetry but may influence total response.
- Many modern electrolytics are not rated to the 500V working level, with power-on levels to 600V as the diode valve typically starts to conduct prior to the remaining amplifier valves (the amplifier has no bleed resistor on the power supply), even with the indirectly heated cathode diode. When caps are used in series, a 47uF 350V radial or axial leaded electrolytic is relatively small in size. Radial leaded electrolytic capacitors of small physical size have negligible self-inductance, and their impedance is low for frequencies out to 1MHz. There is likely to be negligible benefit in bypassing a radial electrolytic cap with a lower valued poly cap, given the voltage and capacitance ratings used in the Williamson amp.
- Metallised polypropylene film caps could be used in place of electrolytics when layout and space is available, as they can allow adequate capacitance voltage rating in a single capacitor. Capacitors like [ICEL's MAB A02 400VAC](#) class B motor run cap have a 600VDC continuous, and 750VDC peak spec, and come in sizes up to 15uF. However, they can exhibit a very significant impedance notch around their first self-resonance (~1MHz) which may not be as benign as an electrolytic capacitor's flat (but higher value) impedance response.

l) Using a different output transformer

- Williamson described the detailed design of the output transformer in his WW articles. Any transformer that varies in any way from that design could affect stability performance at the low and high frequency ends of the frequency spectrum.
- The 1953 Naval test report [41] is indicative of the range of performance that some have experienced. The report indicates that the feedback circuitry was optimised for each transformer in an amp. The Williamson amp was constructed from parts and used 807's, a 250k input pot with 10k grid stopper for input, and had increased C1, C2 and C5 values with a regulated 400VDC supply. The amp was tested with the following transformers:
 - Peerless S-265-Q
 - Partridge WWFB/1.7
 - Partridge CFB/1.7
 - Audio Development 314E
 - Stancor A-8054 (tested default, and with optimised feedback and input)
- The phase shift introduced by the output transformer, both at very low frequency due to the primary inductance, and at very high frequency due to leakage inductance, may require additional stabilisation measures to be applied [38]. Williamson introduced a high frequency shelf network in the 'new improved' 1949 WW articles to alleviate the possibility of high-frequency instability. GEC [38] illustrate the use of a similar low frequency shelf network, and discussed in [37].
- Some people have experienced widely different perceived performance when comparing different output transformers. This may be entirely due to lack of care in checking that each transformer was appropriately set up in a test amplifier, or in the speaker loading used.
 - Some amplifiers operate the output stage into class AB. The output transformer leakage inductance between primary half-windings then becomes an issue as one half-winding stops and starts conducting. In addition, the effective shunt winding capacitance doubles when the other primary half winding stops conducting. Both effects can change the high frequency response. Note the difference in coupling between half primaries for Partridge WWFB and CFB transformers [27], and the discussion in [31].
 - A UL configuration can cause additional couplings that may degrade stability and response, as indicated by [30].
- Known output transformers with 10kΩ P-P primary impedance, and designed for or used in a cloned Williamson amp, or a close variant (note that multiple parallel valves or UL may be better with a different primary impedance) are:
 - Vortexion, UK Series 1

| | | | |
|------------------------|-------------------|-----------------|---|
| o Vortexion, UK | Series 2 | from June 1951 | [1] |
| o Partridge, UK | ? | from Sept 1947 | |
| o Partridge, UK | WWFB | from Aug 1949 | [1] , [27] |
| o Partridge, UK | CFB | from 1951 | [27] |
| o Partridge, UK | T/CFB | from 1954 | [45] |
| o Savage, UK | 2B36 | from Dec 1949 | Ref |
| o Savage, UK | 3C67A | | [1] |
| o Elstone, UK | MR/W | | Ref |
| o Woden, UK | WOT.25 / WOT.26 | from Jun 1949 | Ref |
| o Gilson, UK | WO.1796A | | Ref |
| o Gardners Radio, UK | O.P.735 & O.P.736 | | Ref |
| o Red Line, AUS | AF series | from Dec 1947 | Ref |
| o Ferguson, AUS | OP25 | from Feb 1948 | Ref |
| o Bramco, AUS | HF-4 | | |
| o Beacon Radio, NZ | 48S06 | from July 1948 | Ref1 , Ref2 |
| o Wiseman Electric, NZ | 'Williamson' | from Oct 1953 | Ref |
| o Stancor, USA | A-8054 | | |
| o UTC, USA | LS-63 | | Ref |
| o UTC, USA | LS-60A | | Ref |
| o TRIAD, USA | HSM-81 | | (8kΩ P-P) |
| o Freed, USA | F-1959, KA-10 | | |
| o Jorgen Schou, DK | Type 350 | | Ref |
| o Sansui, Japan | HW-731, HW-733 | from April 1954 | |

m) Adding a speaker output zobel network.

- The Heathkit W-5M from 1955 used a 0.1uF-47Ω speaker output zobel network, with 34kHz corner frequency, to maintain output loading on the amplifier. Heathkit referred to the circuit as the 'tweeter-saver', which allowed un-loaded operation of the amplifier as well as flattening the frequency response and smoothing out the phase variation when loaded with a speaker (compared to a test resistive load).
- An option to control the high frequency response of the transformer when the amplifier output is unloaded or capacitively loaded or loaded by a speaker. As feedback level falls, the default output response can include a peaked region (where gain and phase margins could diminish leading to degraded stability), depending on loading impedance at the frequency of the peak – see [41] and [42].
- A well designed multi-driver speaker system can provide a smooth impedance-frequency characteristic throughout the audio range and beyond. In contrast caution would be required for speakers with uncompensated, high-rate crossover networks.

n) Tuning the first choke CH2 to alleviate mains 2nd harmonic ripple.

- Although not an uncommon technique, this change is not known to have been applied to the Williamson amp in the 1950-60's. www.keith-snook.info
- The choke is bypassed with a capacitor to reduce the 2nd order harmonic output level, but causes an increased level of higher order mains harmonics. Given the likelihood of choke inductance being higher than its rated value when DC current is below the rated level, and given the increase in higher order harmonics with increasing capacitance, it is recommended that a lower capacitor value is used than what would be expected to tune the rated inductance at 2f – perhaps at least 20% lower. A 180nF 630V capacitor has a 118Hz self-resonance with a 10H choke. A 330Ω dampening resistance in series with the capacitor (ie. about twice the choke DCR) is recommended.

- If applied, then the C8 filter capacitor value should be increased to attenuate the higher order mains harmonic levels.
 - Placing a common-mode choke prior to C8, with >100mH differential inductance, may be beneficial in maintaining high series impedance above 10kHz. The choke winding would need suitable insulation. Hum current may bypass the choke due to transformer winding stray capacitance to chassis.
- o) Additional protection items
- Power transformer HT secondary over-current protection.
 - fuse the CT [8] – see section 5.
 - Power supply diode failure protection.
 - SS diode in series with each valve diode anode to reduce PIV stress and arcing due to age, especially if a 5V4 is used (see section 5). Given the 425VAC secondary rating, at least two 1N4007 in series would be needed for each valve diode anode [47].
 - V2 grid-cathode over-voltage protection to reduce stress at power on.
 - Not a commonly reported failure mode, but Vgk is stressed at turn-on, in excess of +450V and up to +600V, until V1 and V2 start conducting.
 - A neon tube (eg. NE2) across grid-cathode clamps voltage to ~100V, and has ~1pF shunt capacitance. Using a 1N4007 may be acceptable, as leakage current is negligible, and junction capacitance rises to about 20pF at zero bias, and so may have no influence at -2V.
 - Output transformer primary winding over-voltage protection.
 - Not a commonly reported failure mode.
 - Windings have low leakage inductance, and class A operation, to alleviate operational over-voltages.
 - Secondary winding has a minor amount of loading from feedback network, and any added zobel network.
 - A MOV across each primary half-winding with a minimum DC 1mA voltage rating of at least about 600V, and no more than about 800V. A resistor in series with the MOV (or series MOVs) could provide an RC filter corner frequency for some additional phase margin. For example, using two 7mm disk 330VDC 90pF part in series would add about 45pF of additional shunt capacitance across each half-primary (or use with a series resistor), which is about an 8% increase in half-primary winding lumped shunt capacitance for a WWFB OT.
 - Topic discussed in [46].
 - Output stage bias protection.
 - The variable resistors R17 and R21 pose a risk from an open wiper. R21 should have the wiper also connected to the unused end terminal. R17 should include an extra resistor from pot wiper to each end terminal.
 - Power supply bleeder.
 - It is always advisable to include a power supply bleeder resistance, to reduce any chance that power supply or coupling capacitors remain charged after the mains supply is disconnected. Voltage balancing resistors across a series connection of electrolytics would achieve that function, as would a resistor divider for an elevated heater supply.
 - Mains AC turn-on stress.
 - An ageing power transformer may be more prone to stress from primary winding in-rush current, at the same time that heater filaments are cold. An NTC thermistor could alleviate that stress.
 - The turn-on timing of the 5V4G may be sufficiently before KT66 conduction starts, causing all B+ rail filter capacitors to be stressed. An NTC thermistor added in series with the 5V4G heater, and designed for 2Arms continuous current with a suitably low voltage drop, can slow the rise of B+ till after KT66 conduction starts. Eg. a CL-21 with a heat-shrink cover.

Note that some commonly applied changes to vintage amplifiers should not be applied without careful

assessment. For example, changing from valve to ss diodes in the power supply may add substantial turn-on stress to the output stage valves, due to the rapid rise in B+ in a shorter time than the CR coupling time-constant, or bypassed cathode time-constant if bypassing is applied.

Some common changes are eminently worthwhile, although diy assessment is needed, and include:

- Power supply secondary fusing and valve diode protection ss diodes.
- Output stage bias adjustment protection.
- Output stage individual valve bias current measurement.
- Power supply bleeder.

9. Setup and Testing

The original articles [1] identify the following procedures to set up correct operating conditions:

- Balanced output stage DC idle currents set by measuring for zero DCV between KT66 plates as R17 is adjusted (assumes output transformer primaries have the same DCR).
- Minimum output stage signal current imbalance with a 400Hz test signal when driving a medium signal level in to a resistive load.
 - Imbalance of gain between V3 x V5, and V4 x V6, will cause asymmetric signal voltages on each primary half-winding of the output transformer. Each valve's voltage gain can be expected to vary by up to about 10%. Even with matched triodes for V3/4, and V5-V6, the distortion can be expected to be tweaked to a lower level.
 - Tested using a sensing transformer primary winding inserted in the B+ lead to the output transformer [48] and listening to a headphone connected to the sensing transformer secondary. Alternatively, measure the AC residual voltage at the common cathode node.
 - Minimising signal imbalance can be achieved using a trimmer resistance across R11 or R13 (similar to pot R12 in the original schematic of the Williamson articles), and possibly a trimmer capacitor across V3 or V4 anode to cathode (when using a high frequency test signal).
- 20dB feedback level confirmed by disconnecting R24 and terminating it to ground via 470Ω and measuring signal voltages. Some ambiguity remains about whether R4 should be bypassed or not.
- Output transformer primary inductance value measurement. Measure AC current with 5VAC mains frequency excitation across total primary winding.

DIY test equipment at the time was typically an [AVO Model 7 multimeter](#), and an oscillator. The meter would allow part resistance and capacitance checking and matching, and circuit operating voltages (at best with 1kΩ/volt loading on the circuit, requiring some care in choosing what to measure, especially around V1, V2).

It is surmised that Williamson used an oscilloscope such as a Cossor 339 to make the signal level measurements for 15W output, as the readings are given as peak voltage ². Only an oscilloscope or a VTVM voltage meter would have had sufficiently high impedance for measuring V2 and V3 grid voltage levels. Few people had access to an oscilloscope in the mid 1940's, and oscilloscope technology was very rudimentary, with no calibrated graticules, or constant impedance inputs yet available, and no probes were provided or available so a direct connection appears to impose about a 1MΩ load.

Nowadays, an oscilloscope and low-distortion waveform generator are typically available for observation of test waveforms, and with sufficient bandwidth in to the 100's of kHz. Typical test techniques include:

- Square and sinewave response assessments with:
 - Changing feedback level
 - Changing load (resistive matched load, no load and capacitance loading)
- Low frequency roll-off measurement:
 - A meter may not be able to adequately measure low frequency response (eg. below 10Hz).

² Alternatively, a VTVM would provide an equivalent high AC impedance load of at least 1MΩ, however an AVO 7 on a low AC voltage range would heavily load the circuit.

- Direct oscilloscope measurement of a square-wave with a 10% droop of the stepped level at a frequency F indicates a -3dB corner frequency of F/30 for a single-pole amplifier response.
- Direct oscilloscope X-Y measurement of output-to-input gain and phase when feedback is disconnected can confirm amplifier response down to below 1Hz.
- High frequency roll-off measurement:
 - A meter may not be able to adequately measure high frequency response (eg. above 50kHz).
 - Direct oscilloscope measurement of a sinewave when feedback is disconnected can confirm amplifier response.
 - Direct oscilloscope X-Y measurement of output-to-input gain and phase when feedback is disconnected can confirm amplifier response.

Testing for low and high frequency stability margins is highly recommended, even though it can be arduous due to the very low and high frequency ranges involved, and the need to confirm across a range of loading (and possibly even secondary winding configurations). A good understanding of gain and phase margins [50],[51],[52], and the influence of remedial networks such as shelf and zobel networks, and the roll-off and resonance behaviour of an output transformer, is required to appreciate what if any circuit modifications may be needed.

Nowadays, PC soundcard or USB interface equipment, as well as custom interfaces, are readily available, and can include and automate detailed and complex audio measurements. Spectrum analysis, harmonic and IM distortion, and noise floor level measurements can be easily achieved with low-cost soundcard and free software. As such, a "modern" Williamson, using matched, stable, modern passive parts and selected valves can be readily tested and should achieve the same performance as Williamson reported.

As a last comment, a hi-fi speaker with 90dB/W/m sensitivity is able to provide an 80dB average listening SPL at 3 meter with 12dB peak-to-average recorded material without exceeding a 15W power capability where waveform clipping starts. For comparison, a very loud cinema type experience may operate up to 85dB average SPL with up to 20dB peak-to-average recorded material.

Thanks to PRR at Hoffman Amps Forum, Dennis Grimwood (www.oestex.com/tubes/) and Patrick Turner during preparation of document, and to John Howes (Howes Acoustics) for Williamson related information.

10. References

- [1] [Williamson 1952 The Williamson Amplifier.pdf.](#)
- [2] [The design of a high fidelity amplifier \(A515\), Radiotronics No.128, 1947.](#)
- [3] [Audio feedback design Part 3, G. Cooper, Radio Electronics, Dec 1950.](#)
- [4] [An analysis of the split-load phase inverter, by G.E. Jones Jr, Audio Engineering, Dec 1951.](#)
- [5] [Analysis of the Williamson Amplifier \(fb_faq7.txt\), Steve Bench.](#)
- [6] Transformer related design and test notes from Patrick Turner's website. <http://www.turneraudio.com.au/>
- [7] Build your own AF valve amplifiers: Circuits for hi-fi and musical instruments, R. Zur Linde.
- [8] [Fusing valve amps.](#)
- [9] ["Improving the Williamson Amplifier" T.M. Wright, Electronics World June 1961.](#)
- [10] [Heathkit W5-M Amplifier Kit, 1955.](#)
- [11] [Building the "Williamson" Amplifier, by H. Kereos, Radio & Television News, December 1950.](#)
- [12] [A High-Quality Audio Amplifier, E.S. Miller, Feb 1952 Radio and Television News.](#)
- [13] [Adapting the "Ultra-Linear" Williamson to 6550 Operation, by Keroes - Radio & Television News, Nov 1955.](#)
- [14] ["Ultra-Linear Operation of the Williamson Amplifier" by Hafler & Keroes, Audio Engineering, June 1952.](#)
- [15] [Amplifiers and Superlatives, by DTN.Williamson & P.J. Walker, WW Sept 1952.](#)

- [16] [Adapting the "Ultra-Linear" Williamson to 6550 Operation](#), by Keroes - Radio & Television News, Nov 1955.
- [17] ["The 'Williamson Type' Amplifier Brought Up to Date"](#) by M. V. Kiebert - August 1952, [Audio Engineering](#).
- [18] [Electronic transformers and circuits](#), R. Lee, 1957.
- [19] [Corrective Networks for Feedback Circuits](#), V. Learned, [Proc. IRE](#), July 1944.
- [20] [Stabilizing feedback amplifiers](#), T. Roddam, [WW Mar 1951](#)
- [21] ["Ultra linear amplifiers, Part 3"](#) by F. Langford-Smith & A. Chesterman, [Radiotronics July 1955](#).
- [22] ["Modernize your Williamson"](#), by Hafler 1956.
- [23] "Valve amplifiers" 3rd edition by Morgan Jones, 2003.
- [24] [KT66 MOV GEC datasheet](#)
- [25] [KT66 Marconi datasheet](#)
- [26] [6SN7GT datasheet](#)
- [27] [Partridge WWFB and CFB datasheets](#)
- [28] [Australian patent 144125 by W.T. Duerdoth, 1948](#).
- [29] ["Some consideration in the design of negative-feedback amplifiers" by W.T. Duerdoth, Proc. IEE - Part III: Radio and Communication Engineering, May 1950](#).
- [30] ["UL output transformers"](#), by D. Leakey and R. Gilson, [WW Jan 1956](#).
- [31] [R.F. Gilson technical specification for WO 1796 and 1796A output transformers](#).
- [32] [Paul Ruby style grid clipper](#).
- [33] [Room EQ Wizard software](#).
- [34] [Distortion in voltage amplifiers](#), by W.B. Bernard, [Audio Engineering](#), February 1953.
- [35] [The importance of balance in push-pull amplifiers](#), by J. Marshall, [Radio Electronics](#), July 1953.
- [36] [6SN7: Driver of choice](#), by E. Barbour, [VTV 11](#), Spring 1999.
- [37] [Rec.audio.tubes thread on Strawman](#), circa 2005.
- [38] ["An approach to audio frequency amplifier design"](#), Appendix B – Output transformers and stabilisation, G.E.C., 1957.
- [39] ["Effect of the Cathode Capacitor on P-P Output Stage"](#), by R.M. Mitchell, p.21, [AUDIO](#), Nov 1955.
- [40] ["Power supply choke measurement"](#), by the author.
- [41] [Laboratory Tests of some of the popular audio amplifiers](#), T.O. Dixon, April 29, 1953 - [NRL Report 4136](#).
- [42] [The 'Linear Standard' Amplifier](#) by J.Z. Knapp in May 1954.
- [43] [The Williamson Amplifier of 1947](#), by P.R. Stinson.
- [44] [Circuit Design Factors for Audio Amplifiers](#), M.V. Kiebert, [Electronics](#), April 1955.
- [45] [Partridge information](#).
- [46] ["Output transformer protection"](#), by the author.
- [47] ["Power supply issues in valve amps"](#), by the author.
- [48] [Chapter 9, page 104, checking for balance section](#), in "Amplifiers – the why and how of good amplification" by G.A. Briggs and H.H. Garner.
- [49] [Universal feedback amplifier circuit](#), A.J. Kauder, [Audio \(Engineering\)](#), Jan 1960.
- [50] [High Fidelity Circuit Design](#), N.H.Crowhurst & G.F.Cooper, 1956.
- [51] [Audio Measurements](#), N.H.Crowhurst, 1958.
- [52] [Stabilizing Feedback Amplifiers](#), N.H.Crowhurst, [Radio Electronics – Audio High Fidelity](#), Dec 1956.