

**Thank you for your interest in our schematics.** The schematic is available on the next page.


If you want to download additional parts of a schematic, or additional schematics, these must be requested individually.

To provide you with this information, more than 6000 members work regularly on the content of Radiomuseum.org.

As a member, you can access schematics, large images without watermarks and collector's prices. You will also surf at Radiomuseum.org without advertising. To do so, you may support Radiomuseum.org with a one-time membership fee of 20 € or 30 CHF or 25 US \$. We would be delighted if you joined as a member:


[https://www.radiomuseum.org/dsp\\_anmelden\\_start.cfm](https://www.radiomuseum.org/dsp_anmelden_start.cfm)
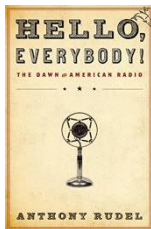
#### These books might be of interest of you:



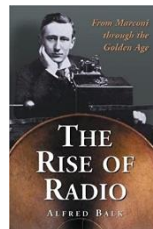
##### **Hello, Everybody! The Dawn of American Radio**

Long before the Internet, another young technology was transforming the way we connect with the world. At the dawn of the twentieth century, radio grew from an obscure hobby into a mass medium with the power to reach millions of people.


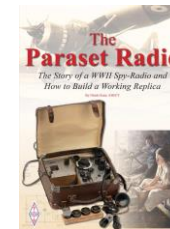
##### **The Rise of Radio, from Marconi through the Golden Age**

As the dominant form of electronic mass communication in the United States from the 1930s into the 1950s, radio helped to forge a modern continental nation. It fused myriad subcultures heavily rural, ethnic, and immigrant into a national identity, unifying the nation in the face of the Depression and war.




##### **The Paraset Radio: The Story of a WWII Spy-Radio and How to Build a Working Replica**

This book describes the gripping story behind the Paraset – a unique spy-radio, dropped behind enemy lines in the dark days of WWII. This radio being both light weight and state of the art for the time was concealed in a suitcase, making ideal for use by the spies of SOE.

Click [here](#) for further information.
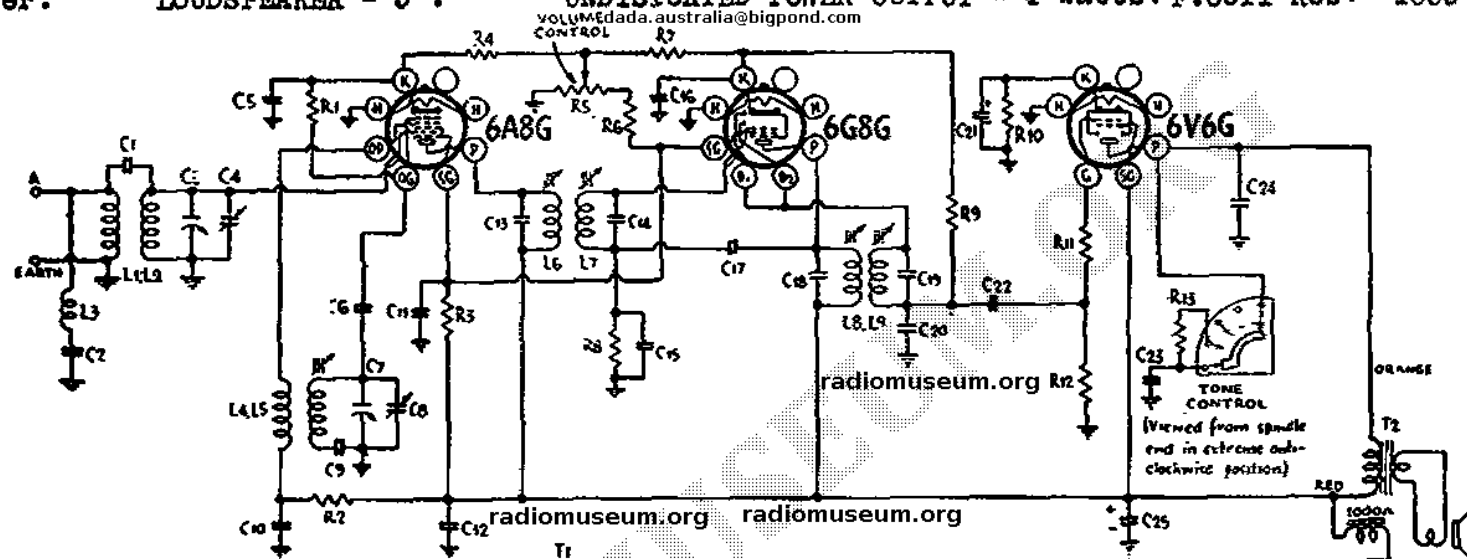
# HOTPOINT-BANDMASTER B64ME & C64ME

TUNING RANGE: 1600-550 Kc/s. R.F. ALIGNMENT SETTINGS: 600 Kc/s. (L.F. Osc.), 1500 Kc. (H.F. Osc. and Aer.) INTERMEDIATE FREQ. - 455 Kc/s. POWER CONSUMPTION - 60 watts. VALVE COMPLEMENT- 6A8G Converter. 6G8G I.F. Amp. and 2nd Det. 6V6G Output. 5Y3G Rectifier. LOUDSPEAKER - 5". UNDISTORTED POWER OUTPUT - 4 watts. F.Coil Res. 1000



- C12-.1mfd paper
- C13-70mmfd Sil.mica
- C14-70mmfd "
- C15-.01mfd pap.
- C16-.1mfd paper
- C17-4mmfd mica
- C18-70mmfd Sil.mica
- C19-70mmfd Sil.mica
- C20-110mmfd mica (L)

Condenser C27, which is not shown in the circuit diagram, is connected between the moving arm of the Volume Control (R5) and ground.

### COILS

- L1, L2- Aerial Coil
- L3, C2- Filter Unit
- L4, L5 -Osc. Coil
- L6, L7- 1st IF trans.
- L8, L9-2nd IF trans.

### TRANSFORMERS

- T1-Power Trans.50-60C
- T1- " " 40C

T2 -Loudspkr.Trans.

### RESISTORS.

- R1-50,000 ohm 1/3W
- R2-20,000 ohm 1W
- R3-20,000 ohm 2W
- R4-300 ohms 1/3W
- R5-4,000 ohm W/W
- Vol. Cont
- R6-40,000 ohm 1W

- C21-25mfd 40V Electro.
- C22-.05mfd paper
- C23-.05mfd paper
- C24-.02mfd paper
- C25-8mfd 525V Dry electro.
- C26-8mfd 500V Wet Electro.
- C27-25mfd 40V el.(not in circuit)

- C3-6-14mmfd air trim.
- C4-Tuning Cond.
- C5-.1mfd paper
- C6-70mmfd mica (n)
- C7-16-24mmfd air trim
- C8-Tuning Cond.
- C9-420mmfd mica Pad.
- C10-.05mfd paper
- C11-.1mfd paper